

EE 101 Inclass Assignment-1

Name: Pokala Mohith

Division: S2

Roll No: 190050084

Pool: G


Assigned Questions: 2.6, 2.7

Question 1 (2.6)

Prove that for a balanced Wheatstone bridge shown below,

$$R_x = (R_2 R_3) / R_1$$

⑥

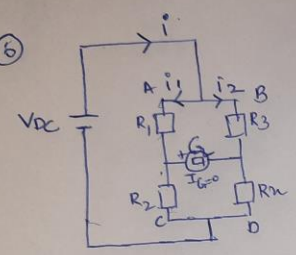


using Kirchhoff's Junction Law
 $i = i_1 + i_2$
and $V_{AC} = V_{BD} = V_{DC}$
 $\Rightarrow i_1 (R_1 + R_2) = i_2 (R_3 + R_x) \rightarrow (1)$
and since Current through Galvanometer = 0
Potential difference across its terminals = 0
 $\Rightarrow i_1 R_1 = i_2 R_3 \rightarrow (2)$

$$\therefore \frac{R_1 + R_2}{R_1} = \frac{R_3 + R_x}{R_3}$$
$$\Rightarrow \frac{R_2}{R_1} = \frac{R_x}{R_3}$$
$$\therefore R_x = \frac{R_2 R_3}{R_1}$$

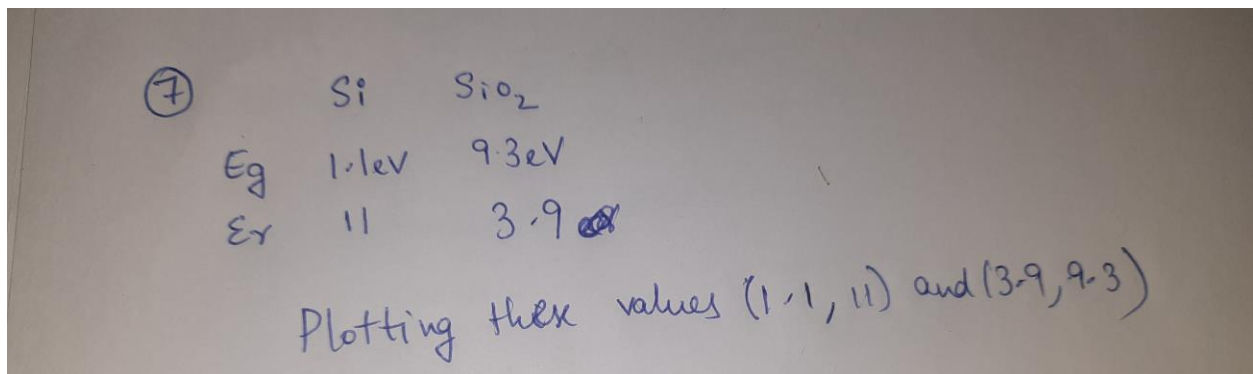Question 2(2.7)


The relative permittivity (ϵ_r) of Si and SiO₂ are 11 and 3.9 respectively. The band gap energy (E_g) of Si and SiO₂ are 1.1eV and 9.3eV respectively at room temperature. Plot the relationship between E_g (x-axis) and relative permittivity (ϵ_r) (y-axis).



Handwritten table and text:

⑦	Si	SiO ₂
E_g	1.1eV	9.3eV
ϵ_r	11	3.9

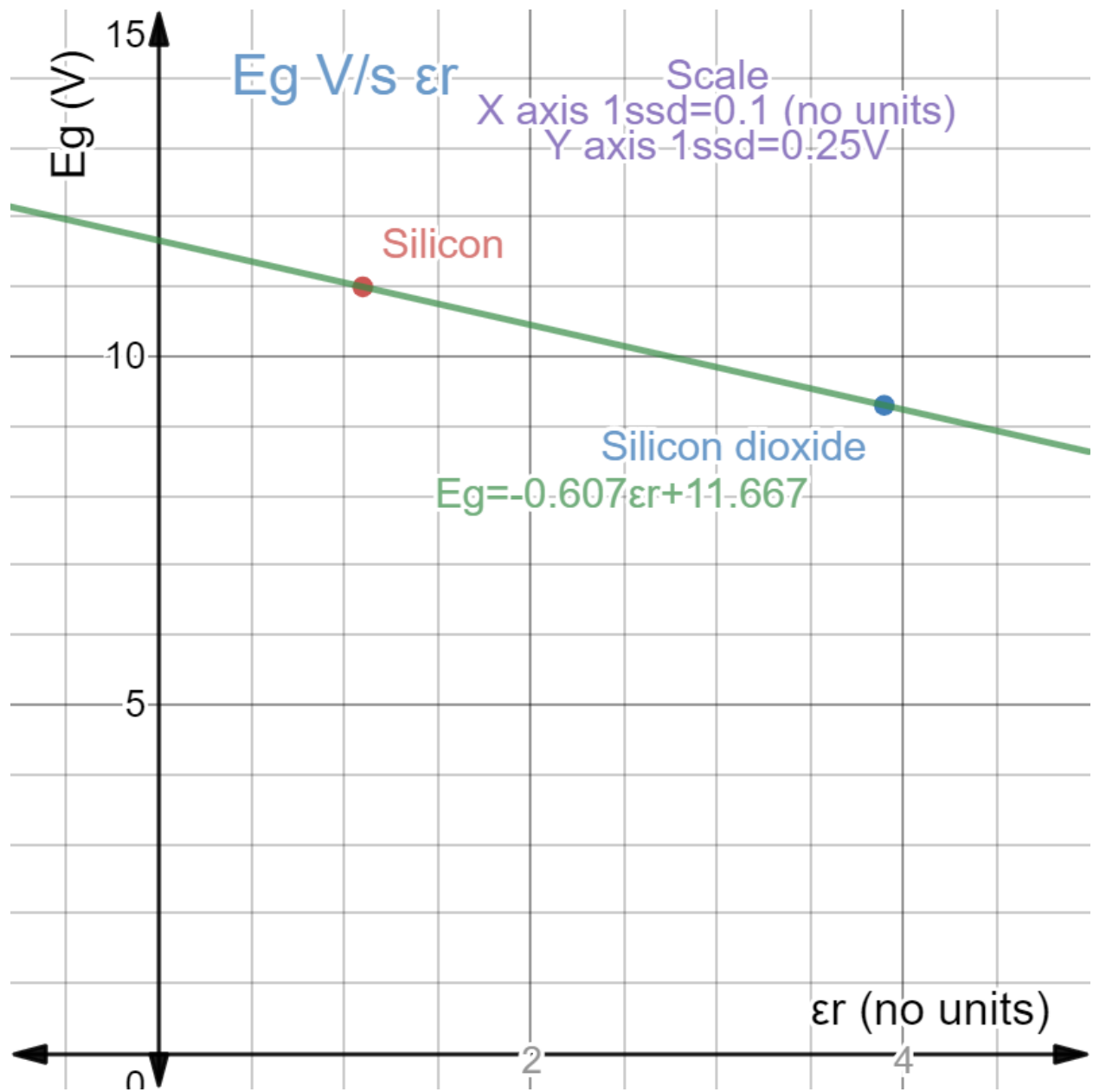Plotting these values (1.1, 11) and (9.3, 3.9)



Plot of E_g (x-axis) and ϵ_r (y-axis).