

EE 101 Tutorial Assignment-1


Name:Pokala Mohith

Division:S2

Roll No:190050084

Pool:G

Question 1:

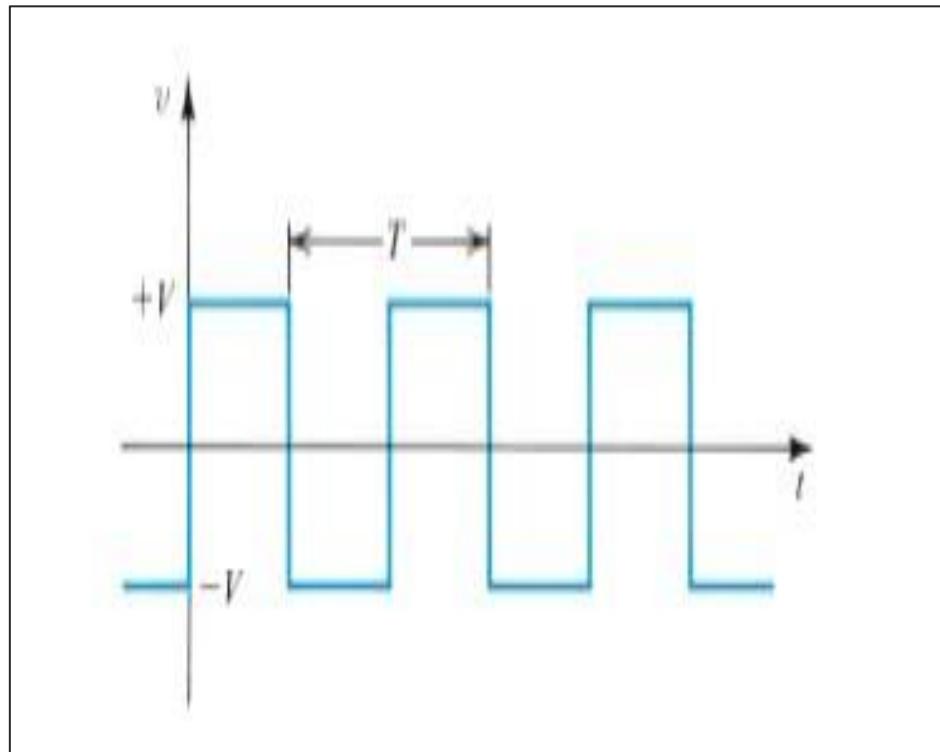

$$v(t) = V \quad (nT \leq t \leq nT + T/2)$$

$$v(t) = -V \quad (nT + T/2 \leq t \leq (n+1)T)$$

By Fourier Transform

$$v(t) = a_0 + \sum_{n=1}^{\infty} a_n \cos\left(\frac{2\pi n}{T}t\right) + b_n \sin\left(\frac{2\pi n}{T}t\right)$$

$$a_0 = \frac{1}{T} \int_0^T v(t) \cos\left(\frac{2\pi n}{T}t\right) dt$$

$$a_n = \frac{2}{T} \int_0^T v(t) \cos\left(\frac{2\pi n}{T}t\right) dt$$

$$b_n = \frac{2}{T} \int_0^T v(t) \sin\left(\frac{2\pi n}{T}t\right) dt$$

$$\begin{aligned}
 a_0 &= \frac{1}{T} \int_0^T v(t) \cos\left(\frac{2\pi n}{T}t\right) dt = \frac{1}{T} \left[\int_0^{T/2} v \cos \frac{2\pi n}{T} t dt - \int_{T/2}^T v \cos \frac{2\pi n}{T} t dt \right] \\
 &= \frac{V}{T} \times \frac{T}{2\pi n} \left[\left[\sin \frac{2\pi n}{T} t \right]_0^{T/2} - \left[\sin \frac{2\pi n}{T} t \right]_{T/2}^T \right] \\
 &= \frac{V}{2\pi} \left[\sin n\pi - \sin 0 - \sin 2n\pi + \sin n\pi \right] = 0
 \end{aligned}$$

$$\begin{aligned}
 a_n &= \frac{2}{T} \int_0^T v(t) \cos\left(\frac{2\pi n}{T}t\right) dt = \frac{2V}{T} \left[\int_0^{T/2} \cos \frac{2\pi n}{T} t dt - \int_{T/2}^T \cos \frac{2\pi n}{T} t dt \right] \\
 &= \frac{2V}{T} \frac{T}{2\pi n} \left[\sin n\pi - \sin 0 - \sin 2n\pi + \sin n\pi \right] = 0
 \end{aligned}$$

$$\begin{aligned}
 b_n &= \frac{2}{T} \int_0^T v(t) \sin\left(\frac{2\pi n}{T}t\right) dt = \frac{2V}{T} \frac{T}{2\pi n} \left[\int_0^{T/2} \sin \frac{2\pi n}{T} t dt - \int_{T/2}^T \sin \frac{2\pi n}{T} t dt \right] \\
 &= \frac{V}{\pi n} \times \left[-\cos n\pi + \cos 0 + \cos 2n\pi - \cos n\pi \right]
 \end{aligned}$$

$$\text{if } n = 2k \text{ then } b_n = \frac{V}{\pi n} \left[-1 + 1 + 1 - 1 \right] = 0$$

$$\text{if } n = 2k+1 \text{ then } b_n = \frac{V}{\pi n} \left[1 + 1 + 1 + 1 \right] = \frac{4V}{\pi n}$$

$$\therefore v(t) = \sum_{k=1}^{\infty} b_{2k+1} \sin \frac{(2k+1)2\pi}{T} t \quad [\text{and } b_{2k}, a_n = 0]$$

$$\therefore v(t) = \frac{4V}{\pi} \left(\sin \frac{2\pi}{T} t + \frac{1}{3} \sin \frac{2\pi}{T} t \times 3 + \frac{1}{5} \sin \frac{2\pi}{T} t \times 5 \dots \right)$$

$$\text{Let } \frac{2\pi}{T} = \omega_0 \therefore \omega_0 = \frac{2\pi}{2\pi/10} = 10$$

$$\therefore v(t) = \frac{4V}{\pi} \left(\sin \omega_0 t + \frac{1}{3} \sin 3\omega_0 t + \frac{1}{5} \sin 5\omega_0 t \dots \right)$$

Fundamental frequency = ω_0 (First harmonic)

~~Fourth~~ ^{Second} ~~Third~~ harmonic has 0 amplitude

Third ~~Second~~ harmonic has $\frac{4V}{3\pi}$ Amplitude

and ^{Fifth} ~~Fourth~~ harmonic has $\frac{4V}{5\pi}$ Amplitude

- a) Identify the first five harmonics of the square wave $v(t)$ expressed in the Fig 1. Consider $V = +2$ Volt, $T = 628$ msec

a) \therefore First five harmonics are

$$\frac{4V}{\pi} \left(\sin \omega_0 t + \frac{1}{3} \sin 3\omega_0 t + \frac{1}{5} \sin 5\omega_0 t \right)$$

b) What fraction of energy of $v(t)$ in its fundamental

(b) We know $E \propto \int_0^T V^2 dt$ (since wave is periodic with time period T)
 Let n th harmonic (n is odd) $= \frac{4V}{n\pi} \sin(n\omega t)$

$$E_n = \frac{16V^2}{n^2\pi^2} \int_0^T \sin^2(n\omega t) dt$$

$$\begin{aligned} & \frac{16V^2}{n^2\pi^2} \times \frac{1}{2} \int_0^T (1 - \cos 2n\omega t) dt \\ &= \frac{8V^2}{n^2\pi^2} \left(T - \frac{\sin 2n\omega T}{2n\omega} \right) \quad [\text{Since } \omega_0 T = 2\pi \Rightarrow \sin 2n\omega T = 0] \\ &= \frac{8V^2}{n^2\pi^2} \times T \\ \therefore E_n \propto \frac{1}{n^2} \Rightarrow E_n = \frac{E_0}{n^2} \end{aligned}$$

$\frac{1}{1^2} + \frac{1}{3^2} + \frac{1}{5^2} + \dots = \frac{1}{1 + \frac{1}{4} + \frac{1}{25} + \dots} = \frac{1}{\pi^2/8} = \frac{8}{\pi^2} \approx 0.81$

fraction in fundamental $= \frac{E_1}{E_0 + E_3 + E_5 + \dots} = \frac{E_0}{E_0 + \frac{E_0}{9} + \frac{E_0}{25} + \frac{E_0}{49} + \dots} = \frac{1}{1 + \frac{1}{9} + \frac{1}{25} + \dots} = \frac{1}{\pi^2/8} = \frac{8}{\pi^2} \approx 0.81$

c) What fraction of energy of $v(t)$ in its first five harmonics?

(c) Energy Present in first five harmonics

$$\begin{aligned} &= \frac{E_0 + \frac{E_0}{9} + \frac{E_0}{25}}{E_0 + \frac{E_0}{9} + \frac{E_0}{25} + \frac{E_0}{49} + \dots} = \frac{\frac{1}{9} + \frac{1}{25}}{\pi^2/8} = 0.81 \left(\frac{1}{9} + \frac{1}{25} \right) \\ &= 0.81 + 0.09 + 0.032 \\ &= 0.932 \end{aligned}$$

d) Till what number of harmonics is 90% of the energy?

(d) First harmonic has 81% of total energy
 Second harmonic has 9% of total energy
 Third harmonic contributes to 9% of total energy
 Number of harmonics which contribute to 90% energy = 3

QUESTION 2

a) Find the time period. and the cyclic and radian frequencies for each of the following sinusoids

$$v_1(t) = 17 \cos(2000t - 30^\circ) \quad v_2(t) = 12 \cos(2000t + 30^\circ)$$

$v_1(t) = 17 \cos(2000t - 30^\circ)$

It is of the form $A \cos(\omega t + \phi)$ where $\omega = 2000 \text{ rad/s}$

We know Time period is $\frac{2\pi}{\omega} = \frac{2\pi}{2000} = \frac{\pi}{1000} = 3.14 \text{ msec}$

Radian frequency $= \omega = 2000 \text{ rad/s}$

Cyclic frequency $= \frac{\omega}{2\pi} = \frac{2000}{2\pi} \approx \frac{1000}{3.14} \approx 318.3 \text{ Hz}$

$v_2(t) = 12 \cos(2000t + 30^\circ)$

Radian frequency $(\omega) = 2000 \text{ rad/s}$

Cyclic frequency $(f) = \frac{\omega}{2\pi} = \frac{2000}{2\pi} \approx 318.3 \text{ Hz}$

Time Period $(T) = \frac{2\pi}{\omega} = 3.14 \text{ msec}$

b) Derive the expression and sketch the graph of $v_3(t) = v_1(t) + v_2(t)$

$$\begin{aligned}
 \textcircled{B} \quad v_3(t) &= v_1(t) + v_2(t) \\
 &= 17 \cos(2000t - 30^\circ) + 12 \cos(2000t + 30^\circ) \\
 &= 17(\cos 2000t \cos 30^\circ + \sin 2000t \sin 30^\circ) + 12(\cos 2000t \cos 30^\circ - \sin 2000t \sin 30^\circ) \\
 &= 29 \cos 2000t \cos 30^\circ + 5 \sin 2000t \sin 30^\circ \\
 &= \frac{29\sqrt{3}}{2} \cos 2000t + \frac{5}{2} \sin 2000t
 \end{aligned}$$

Let $\omega t \phi = \left(\frac{29\sqrt{3}}{5}\right) \Rightarrow \phi = \cot^{-1}\left(\frac{29\sqrt{3}}{5}\right) = 5.69^\circ$

$$L(t(v_3 t)) = A \cos \phi \cos(2000t) + A \sin \phi \sin 2000t$$


$\Rightarrow A$

$$\text{We Know } \phi = 5.69^\circ$$

$$A \cos \phi = \frac{29\sqrt{3}}{2}$$

$$A = \frac{29\sqrt{3}}{2 \cos(5.69)} = 25.2$$
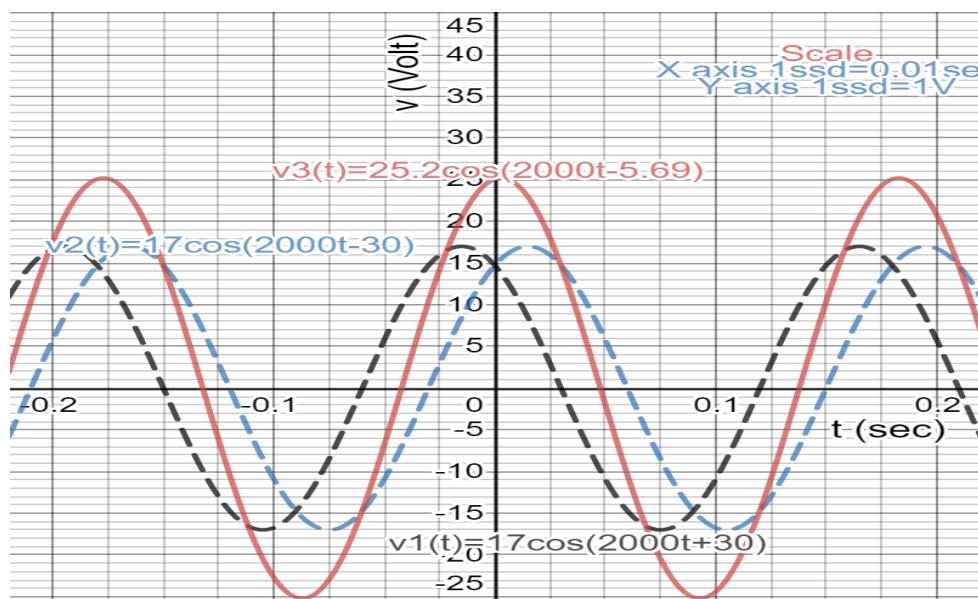
$$\therefore v_3 t = 25.2 (\cos(2000t - \phi)) = 25.2 \cos(2000t - 5.69)$$



Plot of $v_3(t)$ versus time

Question 3

Graphically sketch the waveform described by $v(t) = r(t)/T_c \cdot e^{-t/T_c} u(t)$ Volt [Graph Paper Preferred] $V_A = 1$ Volt, $T_c = 1$ sec


$$v(t) = \frac{r(t)}{T_c} [V_A e^{-t/T_c}] u(t)$$

We know $r(t) = t$ for $t > 0$
 $r(t) = 0$ for $t \leq 0$

$u(t) = 1$ for $t > 0$
 $u(t) = 0$ for $t \leq 0$



$\therefore v(t) = \frac{t}{T_c} V_A e^{-t/T_c}$ volt for $t > 0 = t e^{-t}$ [since $V_A = 1$ Volt, $T_c = 1$ sec]

$$= 0 \quad \text{for } t \leq 0$$

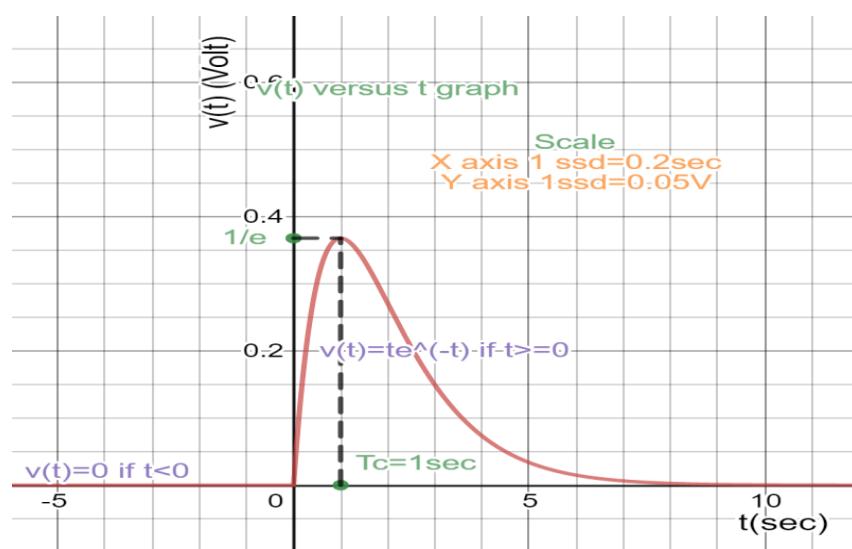


Plot of $V(t)$ versus time(t)

Question 4

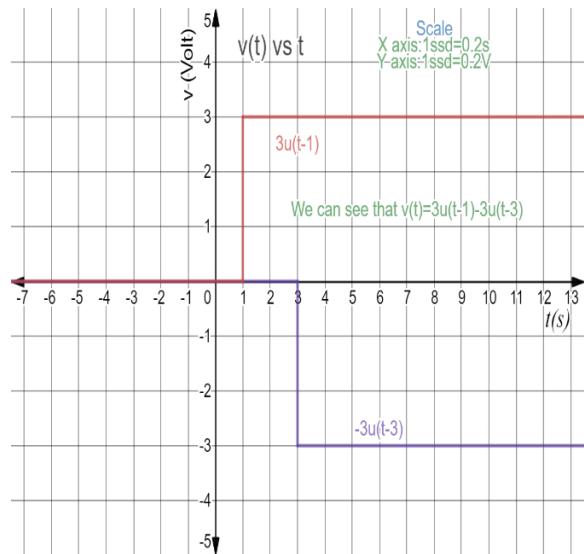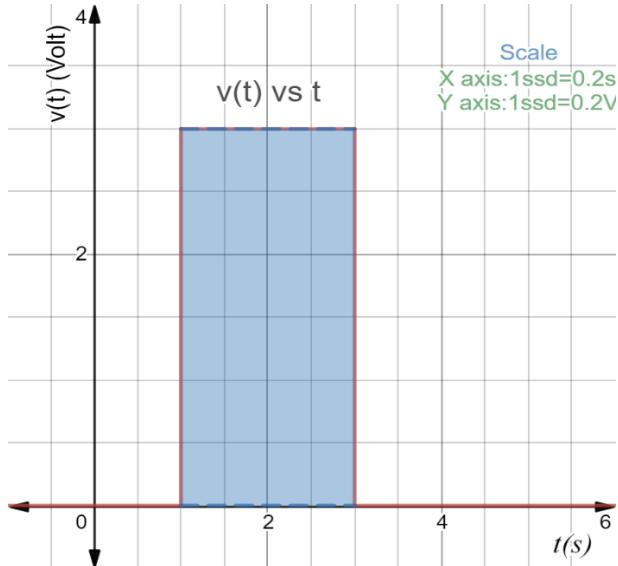


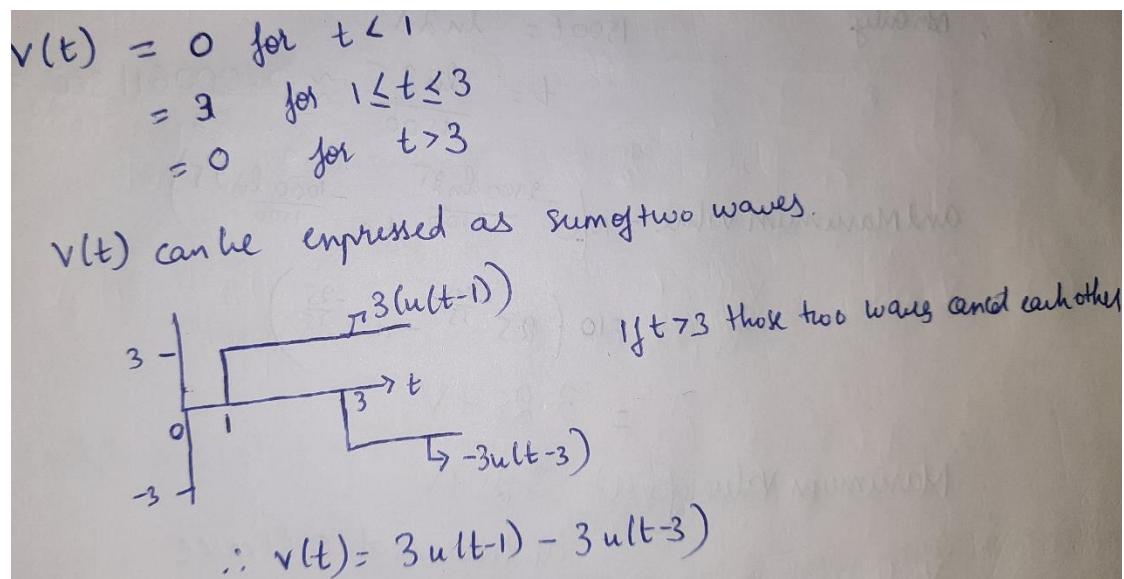a) Express the Gated Pulse Waveform of Fig.2 in terms of Step functions $u(t)$.



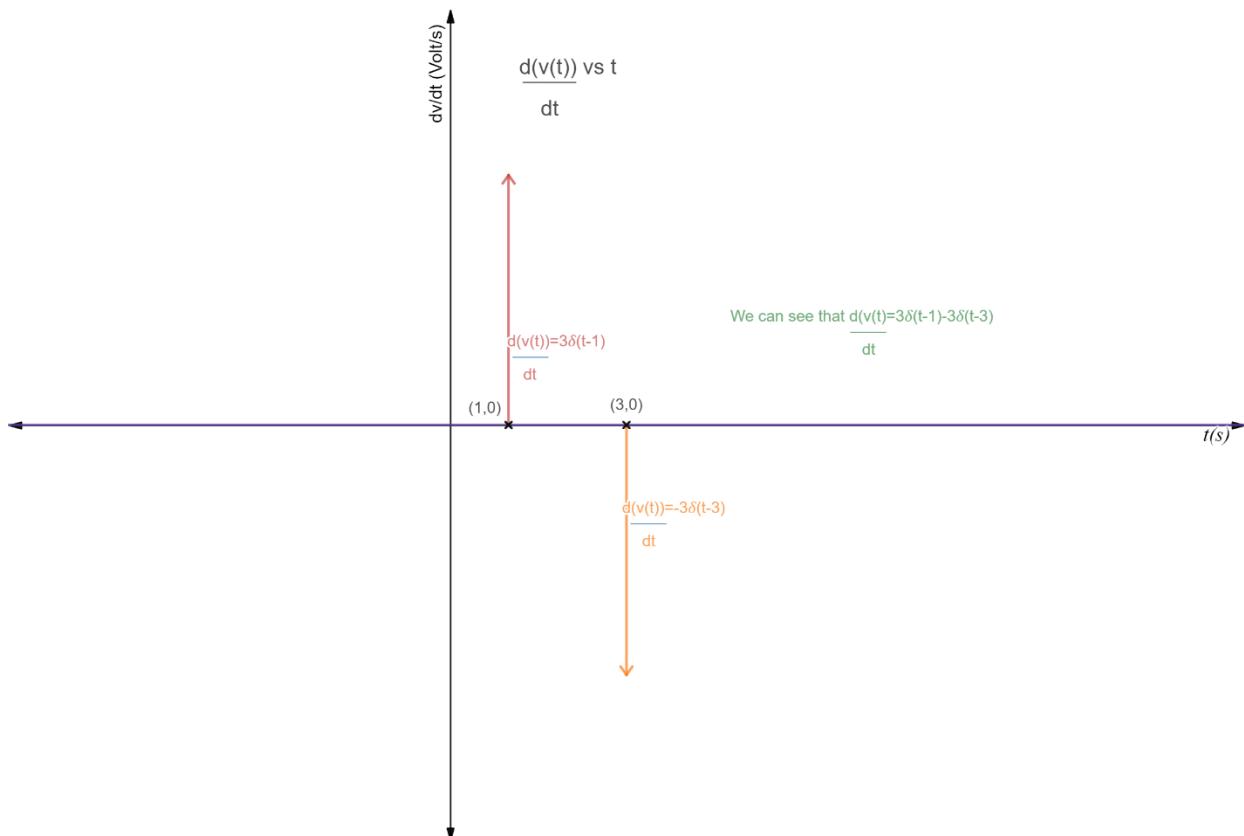b) Determine the expression and graphically sketch the derivative of the gated pulse waveform shown in Fig.2

$$\textcircled{b} \quad \frac{\partial}{\partial t} v(t) = \frac{\partial}{\partial t} 3u(t-1) - 3u(t-3) \\ = 3\delta(t-1) - 3\delta(t-3)$$



Plot of $d(v(t))/dt$ versus time

c) Determine the expression and graphically sketch the integral of the gated pulse waveform shown in Fig.2


(c)

$$v(t) = 3u(t-1) - 3u(t-3)$$

$$\int_{-\infty}^t v(t) dt = \int_{-\infty}^t [3u(t-1) - 3u(t-3)] dt$$

$$= 3[r(t-1) - r(t-3)]$$


where $r(t) = \int_{-\infty}^t u(t) dt$

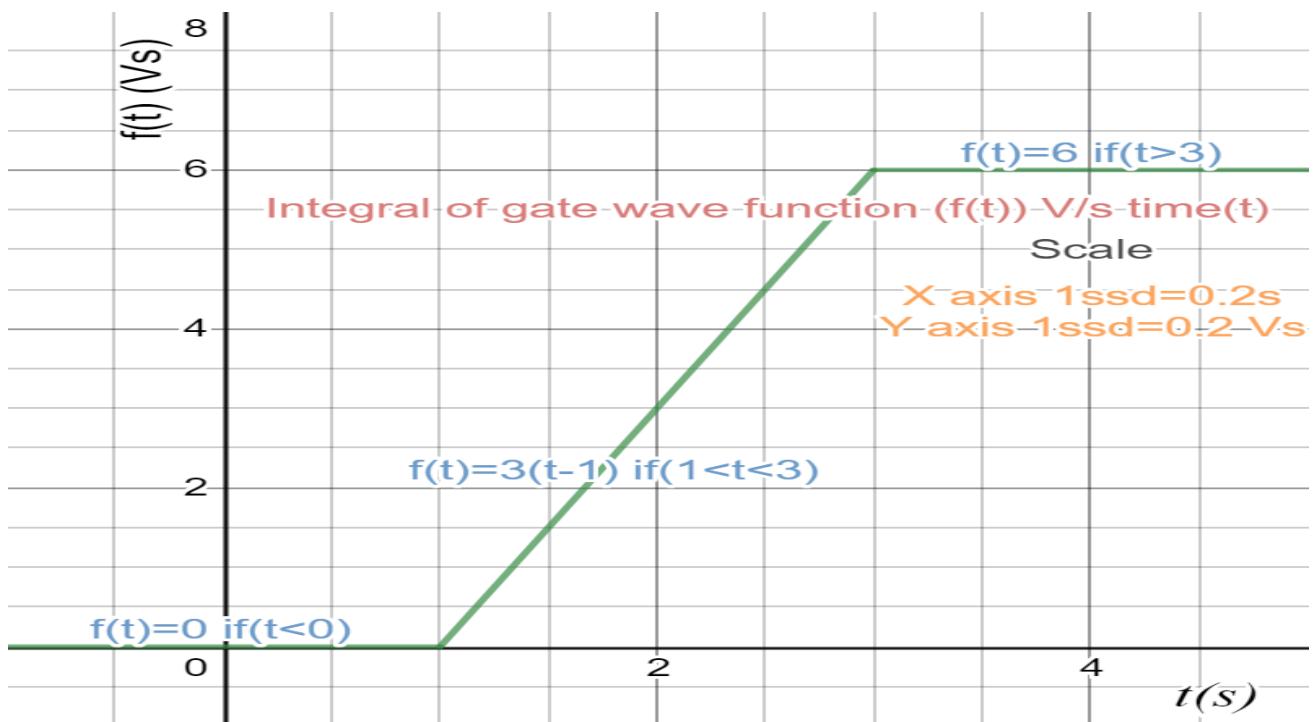

Plot of integral of $v(t)$ versus time

Question 5

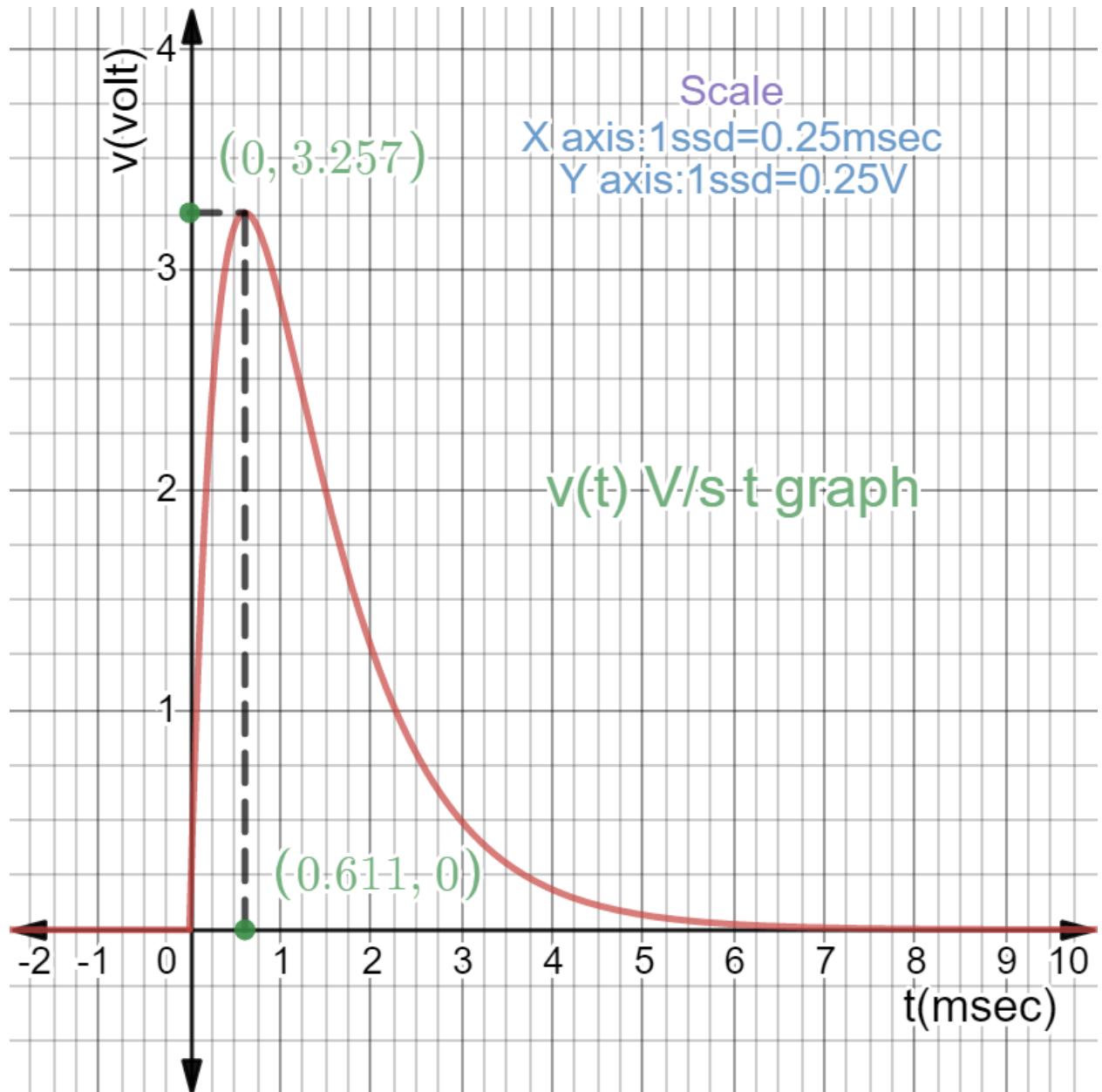a) Plot $v(t)$ expressed by $v(t) = 10 [e^{-1000t} - e^{-2500t}] u(t)$



b) What is the value of $v(t)$ at the extremum and the time when it occurs?

$$v(t) = 10(e^{-1000t} - e^{-2500t})u(t)$$

at ^{global}
^{local extrema} either $\frac{dv(t)}{dt} = 0$ (or) $v(t)$ is discontinuous

$$v(t) = 10(e^{-1000t} - e^{-2500t}) \quad t > 0$$

$$v(t) = 0 \quad t < 0$$

$$\frac{dv}{dt} = 10\left(\frac{2500}{200}e^{-2500t} - e^{-1000t}\right)$$

$$\text{Maximum occurs when } e^{-2500t} = \frac{1}{25}e^{-1000t} \\ e^{1500t} = 25$$

$$t = \frac{\ln 25}{1500} \approx 0.000611 \text{ sec} = 6.1 \times 10^{-4} \text{ sec} \\ \approx 0.61 \text{ msec}$$

$$\text{and Maximum value} = 10\left(e^{-\frac{2500 \ln 25}{1500}} + e^{-\frac{1000 \ln 25}{1500}}\right)$$

$$= 10\left(2.5^{-\frac{10}{15}} - 2.5^{-\frac{25}{15}}\right)$$


$$\approx 3.257V$$

\therefore Maximum value of $v(t) = 3.257V$
 and it occurs at 0.61 msec


Question 6

Find the equivalent resistance seen from terminal A-B using Y - Δ transformation in Fig. 3

$$R_L = 10 \Omega$$

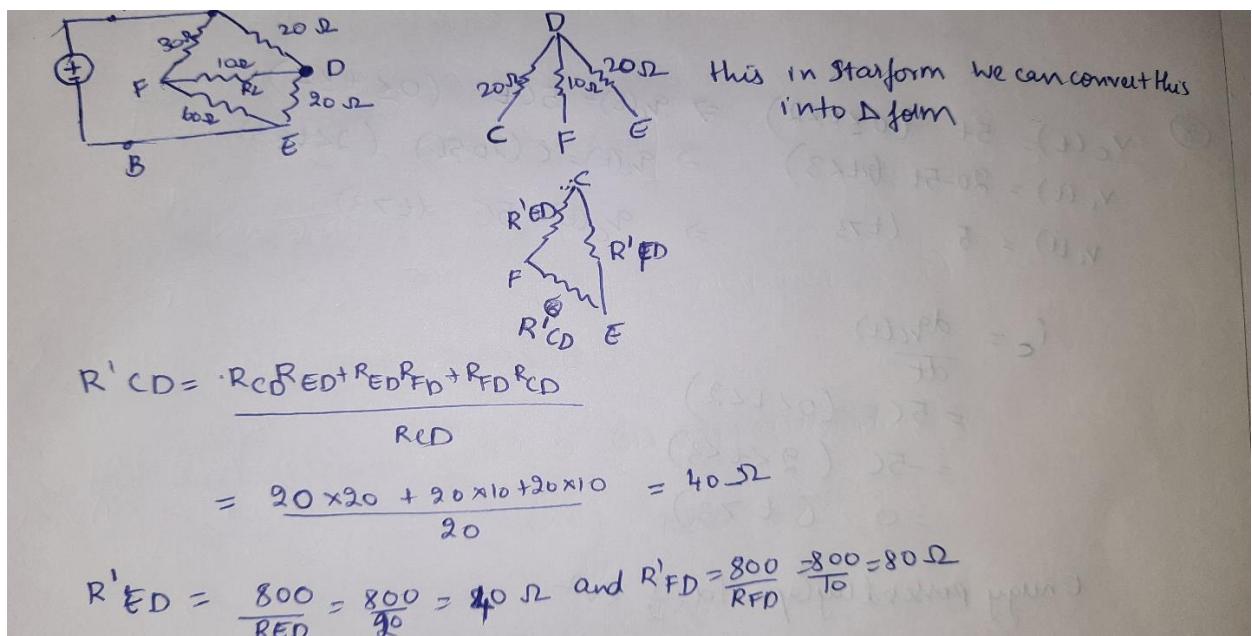

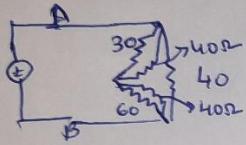\therefore Equivalent Circuit between A and B can be represented as



Between C and F we have two Resistors R_{CF} and R'_{ED} in parallel

$$R_{CF\text{eff}} = \frac{1}{\frac{1}{30} + \frac{1}{40}} = \frac{40 \times 30}{70} = \frac{120}{7} \Omega$$

Between F and E there are two Resistors R_{EF} and R'_{CD} in parallel


$$R_{EF\text{effective}} = \frac{1}{\frac{1}{60} + \frac{1}{40}} = \frac{60 \times 40}{100} = 24 \Omega$$

$$R_{AB} = R_{CE} = \frac{1}{\frac{1}{80} + \frac{1}{24 + \frac{120}{7}}} = \frac{1}{\frac{1}{80} + \frac{7}{288}} = \frac{288 \times 80}{288 + 560} = \frac{288 \times 80}{848} = 27.169 \Omega$$

$$\therefore R_{AB} = 27.169 \Omega$$

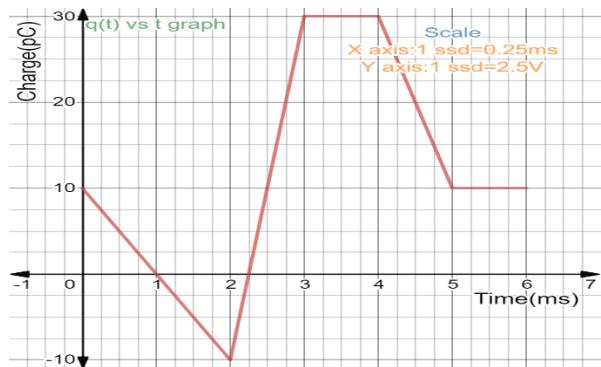QUESTION 7

The graph shows the charge $q(t)$ flowing past a point in a wire as a function of time



$$@ i(t) = \frac{dq(t)}{dt}$$

$$q_1(0 < t \leq 2) = 10 - 10t \Rightarrow i(0 < t \leq 2) = -10 \text{ pC/ms} = -10 \text{nA}$$

$$q_2(2 < t \leq 3) = 40t - 90 \Rightarrow i(2 < t \leq 3) = 40 \text{nA}$$

$$q_3(3 < t \leq 4) = 30 \Rightarrow i(3 < t \leq 4) = 0 \text{nA}$$

$$q_4(4 < t \leq 5) = 110 - 20t \Rightarrow i(4 < t \leq 5) = -20 \text{nA}$$

$$q_5(5 < t \leq 6) = 10 \Rightarrow i(5 < t \leq 6) = 0 \text{nA}$$

\therefore The graph can be plotted now using these values


a) Sketch the variation of $i(t)$ versus time

Plot of $i(t)$ versus time(t)

Scale:

X-axis: 1 small square = 0.25 ms

Y-axis: 1 small square = 2.5 microampere

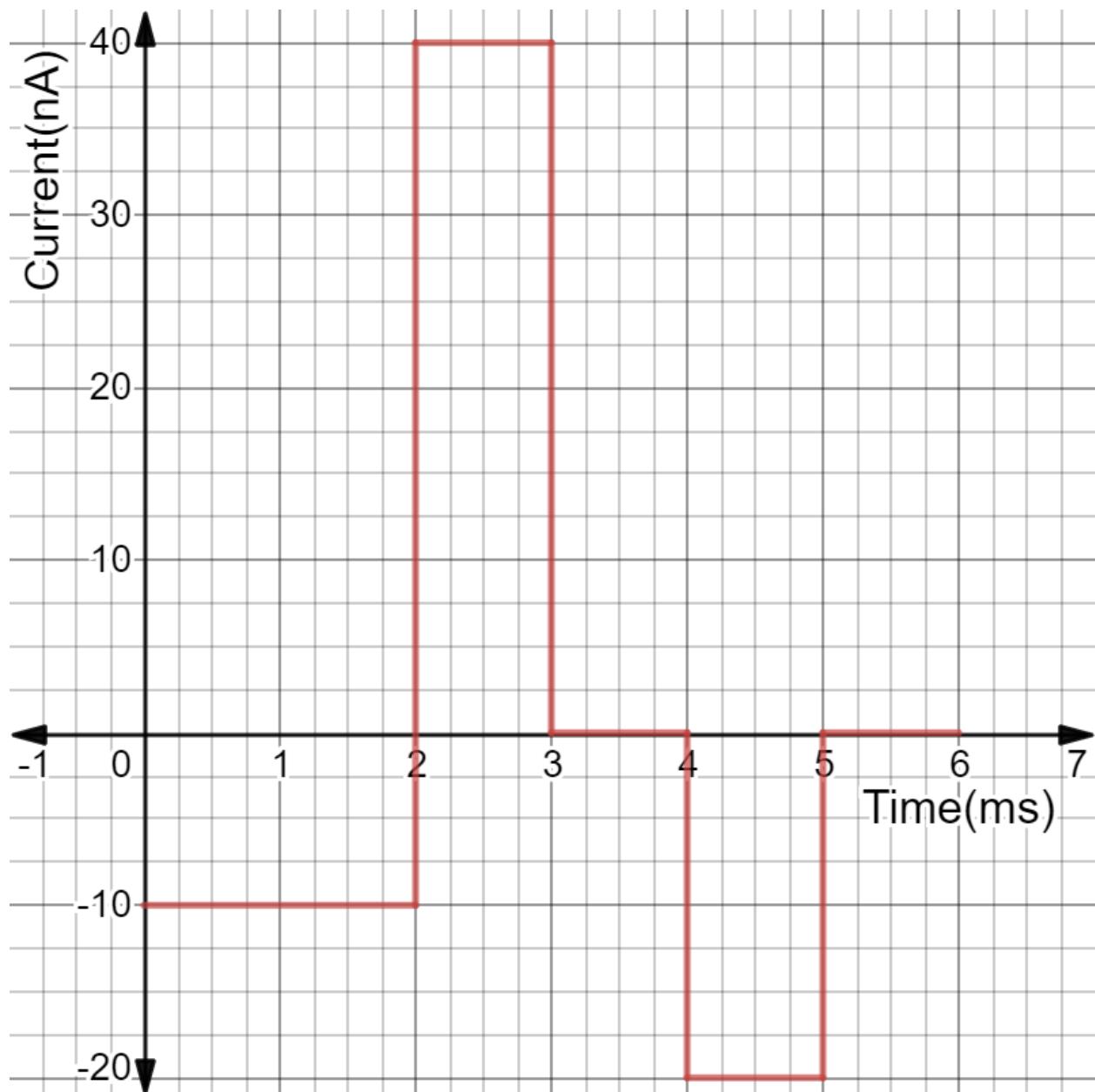


b) Find the current $i(t)$ at 1; 2.5; 3.5; 4.5, and 5.5 msec

$$\begin{aligned}
 \textcircled{b} \quad \therefore i(t=1\text{m}) &= -10\text{nA} \Rightarrow |i(t)| = 10\text{nA} \\
 i(t=2.5\text{ms}) &= 40\text{nA} \Rightarrow |i(t)| = 40\text{nA} \\
 i(t=3.5\text{ms}) &= 0\text{nA} \Rightarrow |i(t)| = 0\text{nA} \\
 i(t=4.5\text{ms}) &= -20\text{nA} \Rightarrow |i(t)| = 20\text{nA} \\
 i(t=5\text{ms}) &= 0\text{nA} \Rightarrow |i(t)| = 0\text{nA}
 \end{aligned}$$

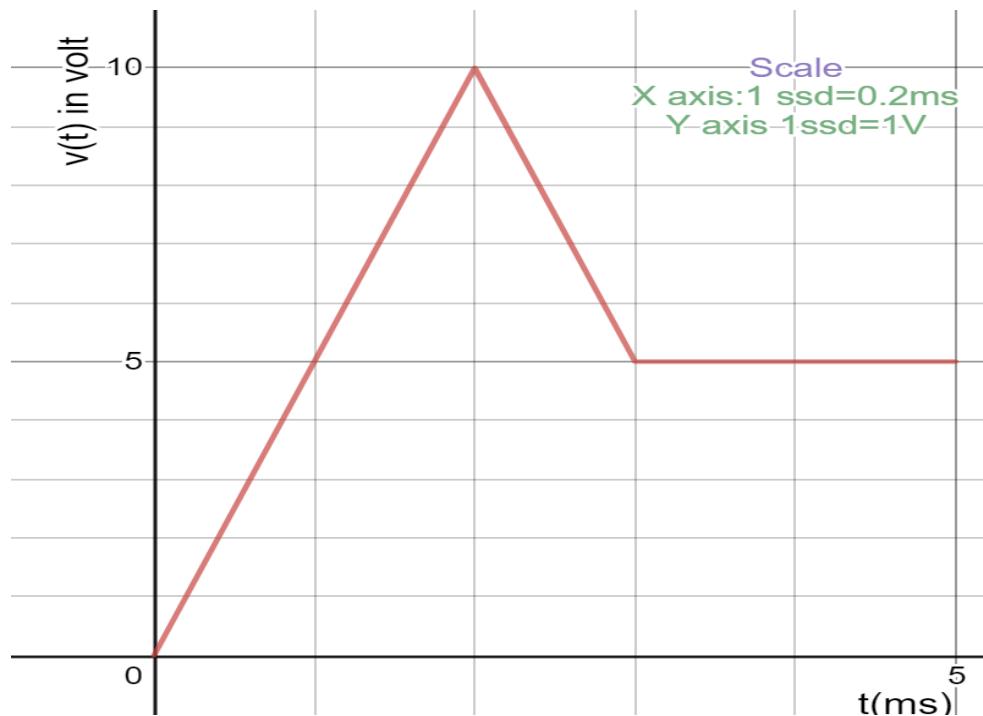Question 8

Below Figure shows the voltage across a $0.5-\mu\text{F}$ capacitor. Determine the time varying current, energy and power of the capacitor



$$\textcircled{8} \quad v_c(t) = 5t \quad (0 \leq t \leq 2) \Rightarrow q_c(t) = 5Ct \quad (0 \leq t \leq 2)$$

$$v_c(t) = 20 - 5t \quad (2 < t \leq 3) \Rightarrow q_c(t) = C(20 - 5t) \quad (2 < t \leq 3)$$

$$v_c(t) = 5 \quad (t > 3) \Rightarrow q_c(t) = 5C \quad (t > 3)$$

$$i_c = \frac{dq_c(t)}{dt}$$

$$= 5C \quad (0 \leq t \leq 2)$$

$$= -5C \quad (2 < t \leq 3)$$

$$= 0 \quad (t > 3)$$

Energy possessed by capacitor = $\frac{1}{2} CV^2$


$$E_c(t) = \frac{1}{2} C(5t)^2 \quad (0 \leq t \leq 2)$$

$$= \frac{1}{2} C(20 - 5t)^2 \quad (2 < t \leq 3)$$


$$= \frac{1}{2} C(5)^2 \quad (3 < t)$$

$$P_c(t) = \frac{d(E_c)}{dt} = \frac{d}{dt}\left(\frac{q^2}{2C}\right) = \frac{qi}{C}$$

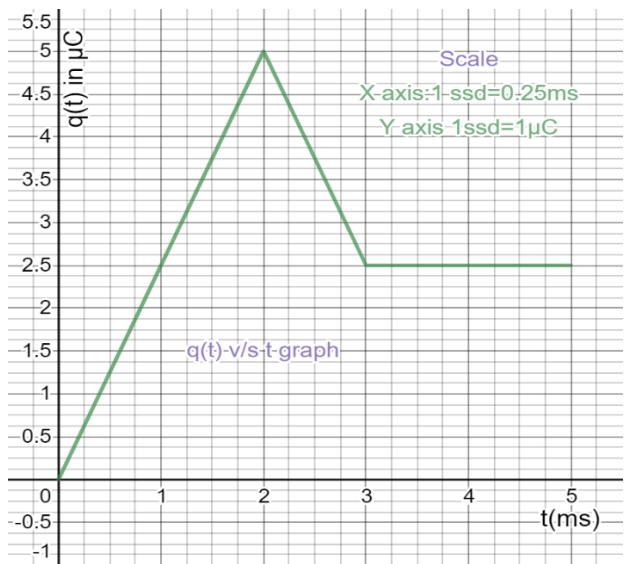
$$\therefore P_c(t) = \begin{cases} 5 \times 5Ct & 0 \leq t \leq 2 \\ 5C(20 - 5t) & 2 < t \leq 3 \\ 5 \times 5C \times 0 = 0 & 3 < t \end{cases}$$




Plot of $q(t)$ versus t

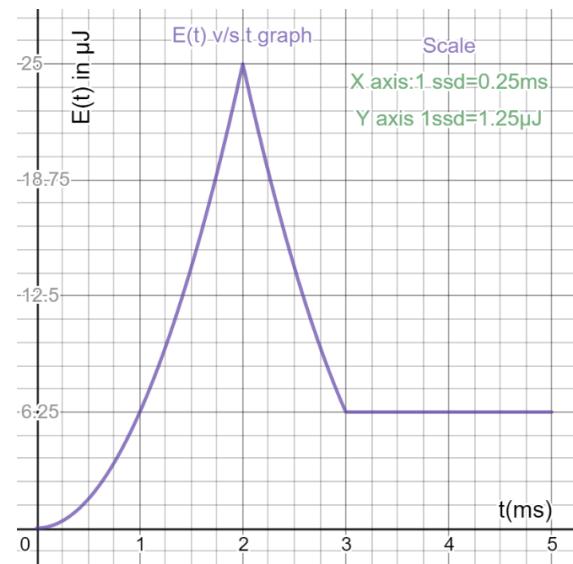

Plot of $E(t)$ versus t

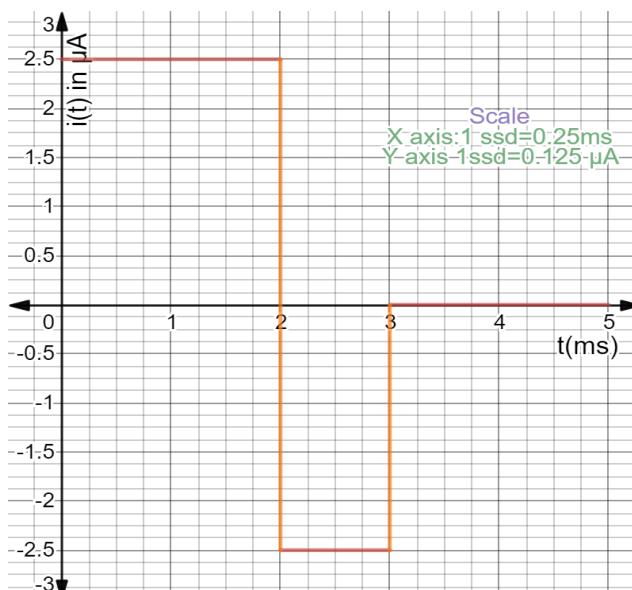

Plot of $i(t)$ versus t

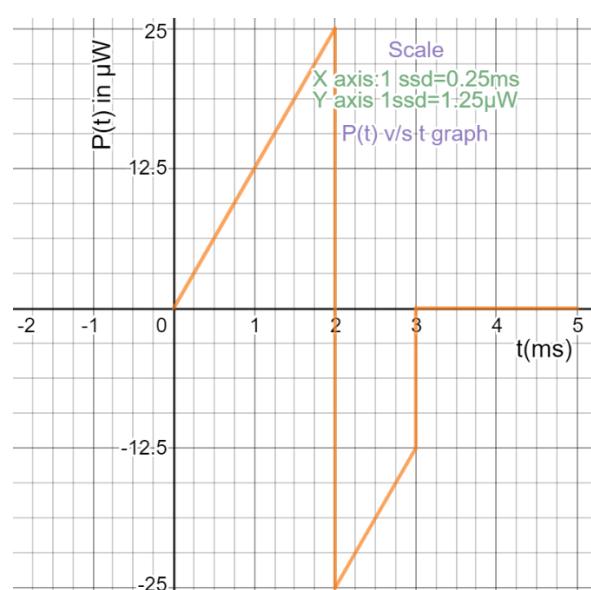

Plot of $P(t)$ versus t

Question 9

The current through a 2.5-mH inductor $i(t) = 10 e^{-500t} \sin(2000t)$. Plot the waveforms of the element current, voltage, power, and energy.

⑨

$$i(t) = 10 e^{-500t} \sin(2000t)$$

$$L = 2.5 \text{ mH}$$

$$V = -L \frac{di}{dt}$$

$$= -2.5 \times 10^{-3} \times \left(\frac{d}{dt} (10 e^{-500t} \sin 2000t) \right)$$

$$= -2.5 \times 10^{-2} (e^{-500t} \times 2000 \cos 2000t - 500 e^{-500t} \sin 2000t)$$

$$= -2.5 \times 10^{-2} \times 500 e^{-500t} (4 \cos 2000t - \sin 2000t)$$


$$= -12.5 e^{-500t} (4 \cos 2000t - \sin 2000t) \checkmark$$

$$\text{Power (P)} = -L i \frac{di}{dt}$$


$$= -2.5 \times 10^{-3} \times 10 e^{-500t} \sin(2000t) e^{-500t} (4 \cos 2000t - \sin 2000t) \checkmark$$

$$E = \frac{1}{2} L i^2$$

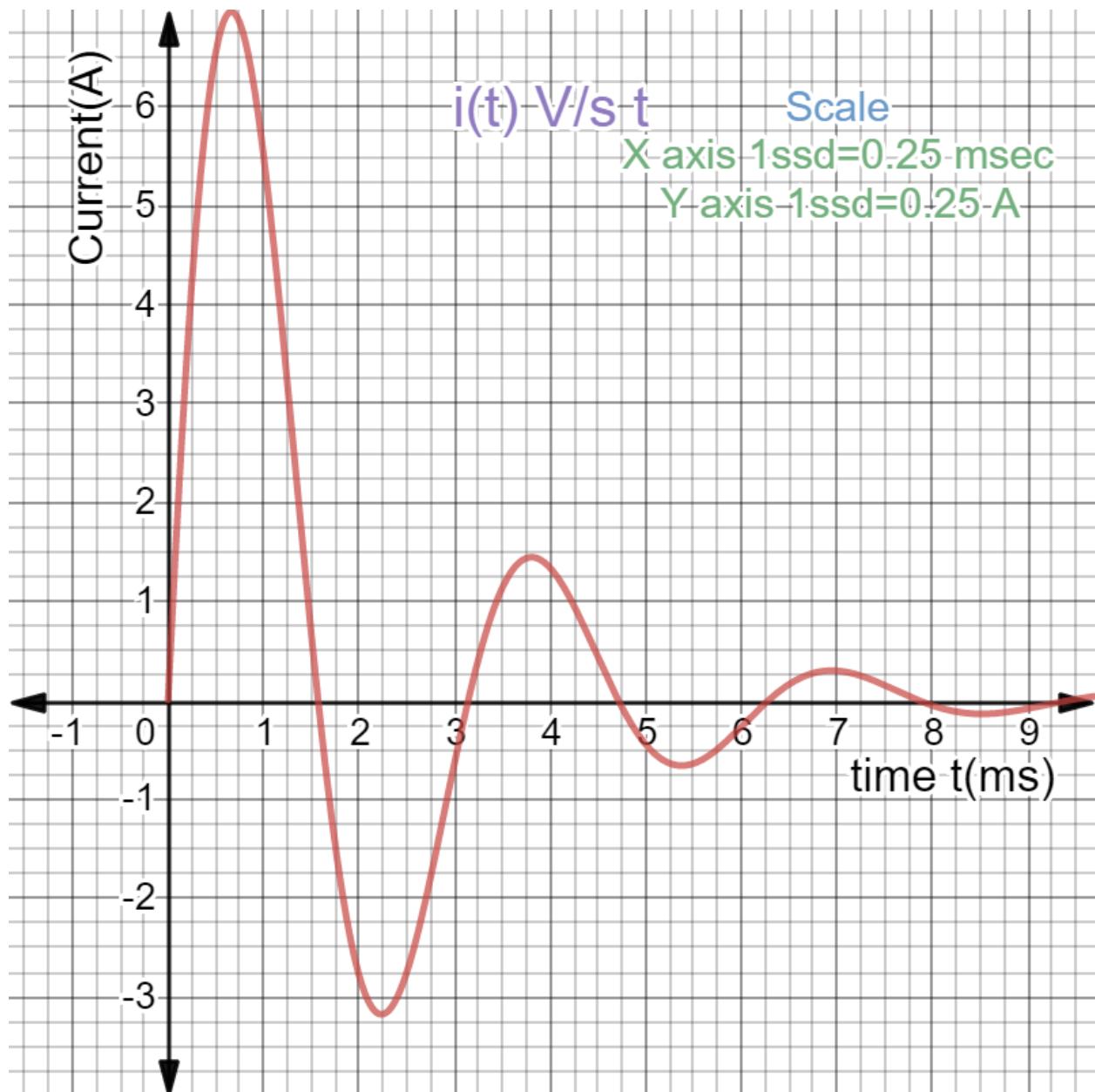
$$= \frac{1}{2} \times 2.5 \times 10^{-3} \times (10 e^{-500t} \sin 2000t)^2$$




Plot of $i(t)$ versus t

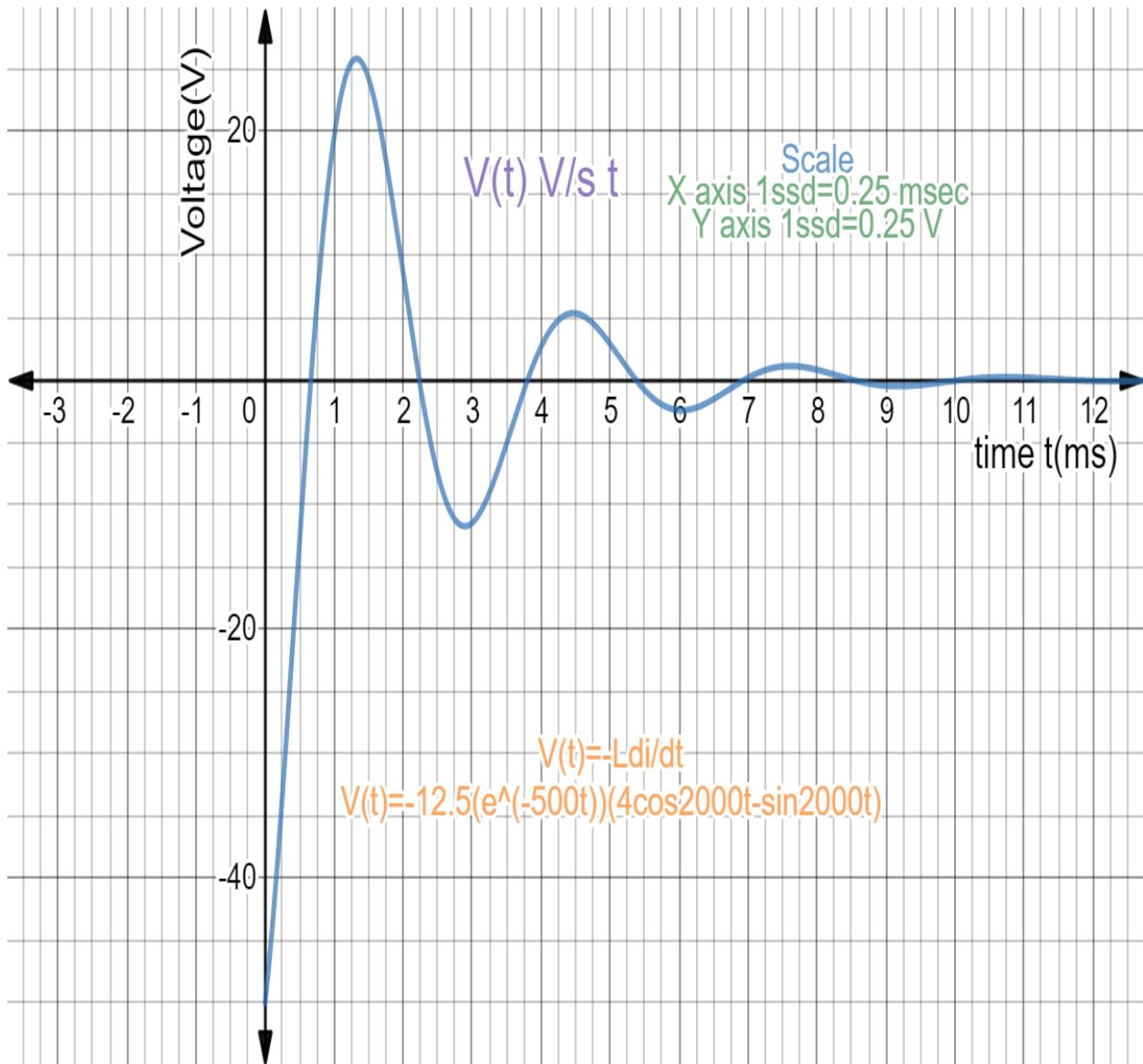

Plot of $V(t)$ versus t

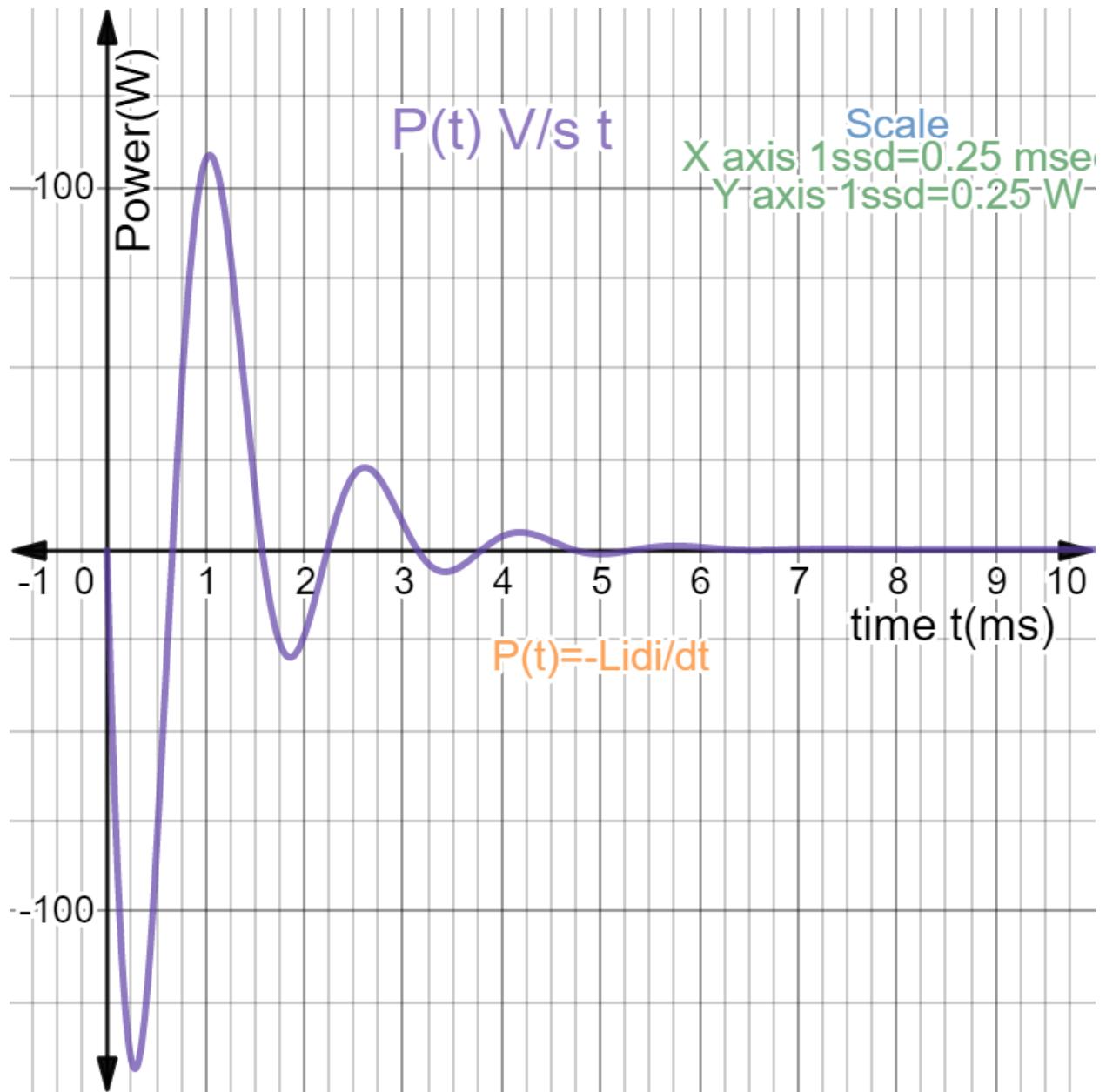


Plot of $P(t)$ versus t

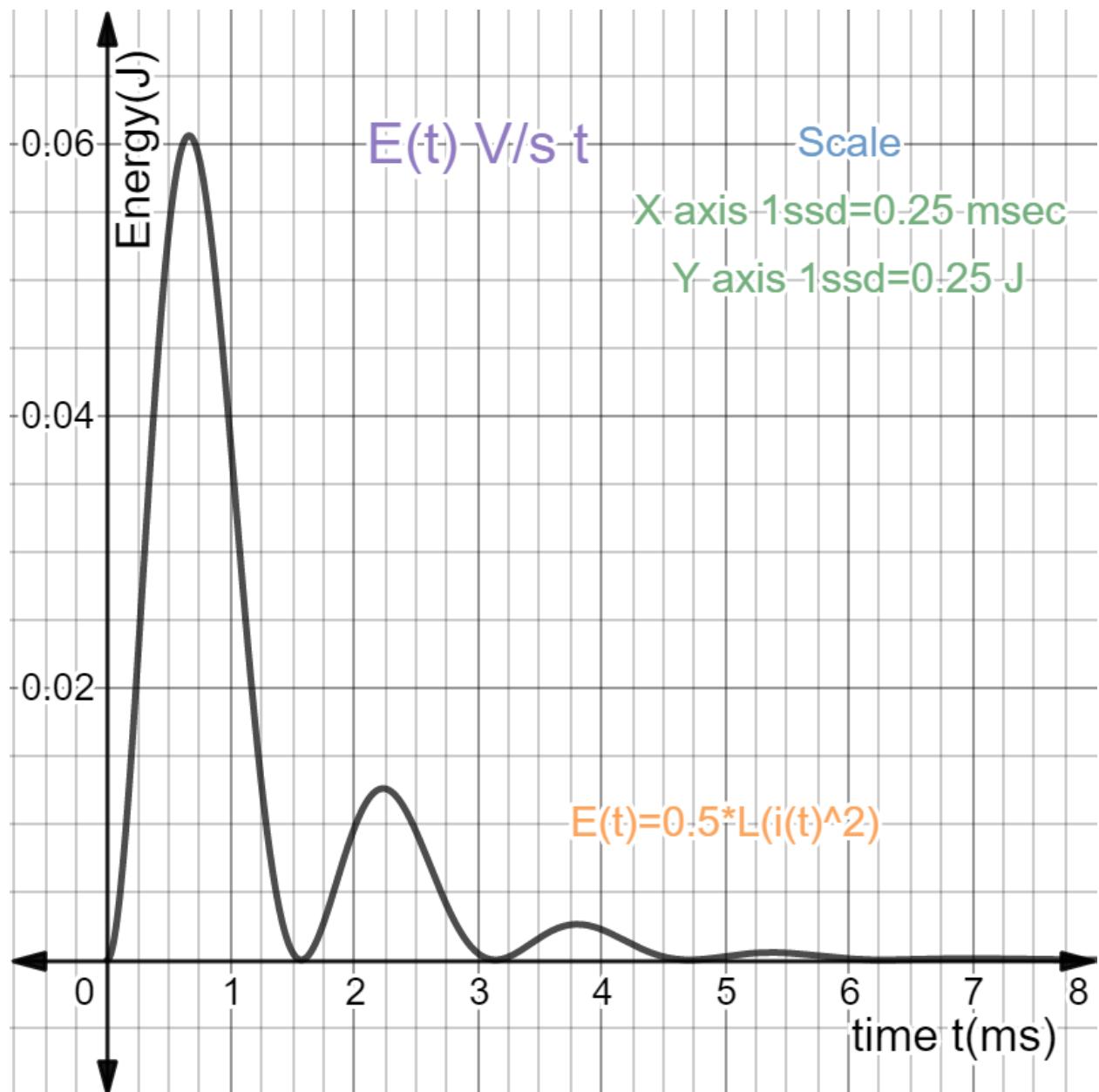


Plot of E(t) versus t

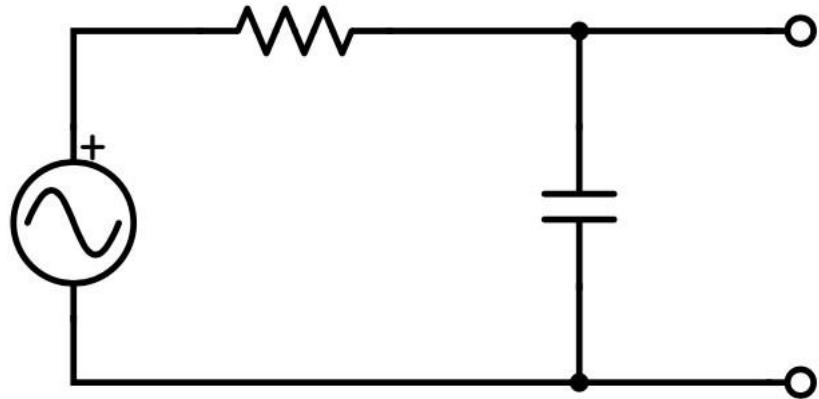Question 10

For the first-order low pass filter as shown below,



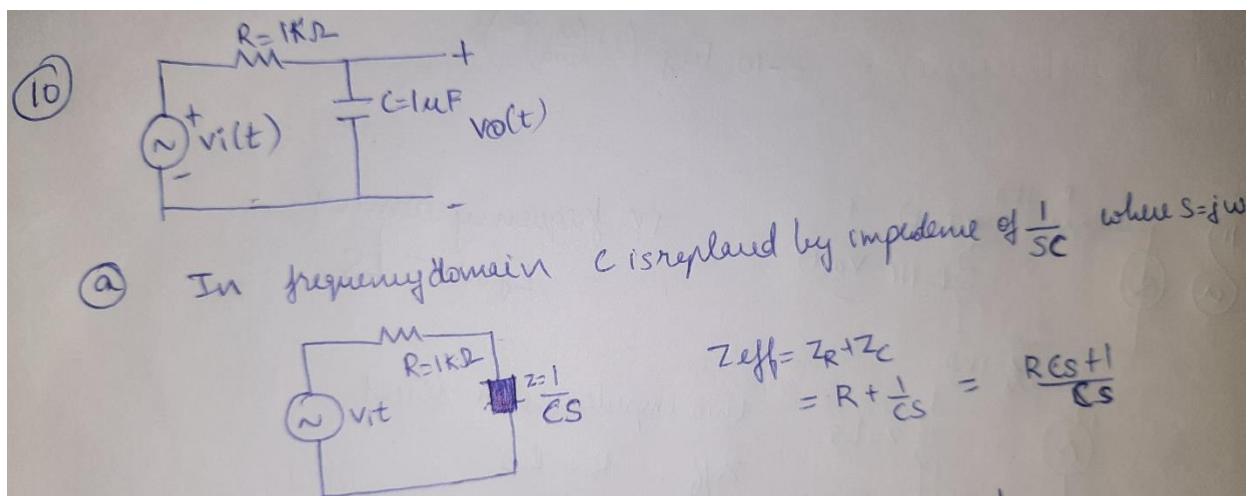- a) Draw s-domain transformed circuit for the filter.



- b) Find transfer function in s-domain i.e $T(s) = V_o(s) / V_i(s)$.

$$(b) T(s) = \frac{V_o(s)}{V_i(s)} = \frac{\frac{1}{sC}}{\frac{1}{sC} + \frac{1}{R}} = \frac{\frac{1}{sC}}{\frac{1}{R} + \frac{1}{sC}} = \frac{1}{sC + \frac{1}{R}}$$

C) Hence find transfer function for physical frequencies i.e $T(j\omega)$ by $s = j\omega$ and derive expression for magnitude response, $|T(j\omega)|$

$$\textcircled{c} \quad T(j\omega) = \frac{1}{Rc j\omega + 1} \quad (s=j\omega)$$

$$|T(j\omega)| = \frac{1}{\sqrt{1+(Rc)^2\omega^2}}$$

$$|T(j\omega)| = \frac{1}{\sqrt{1+(\omega/\omega_0)^2}}$$

$$\omega_0 = \frac{1}{Rc}$$

d) Also calculate the 3-dB frequency or corner frequency, ω_0 for the filter

$$\textcircled{d} \quad \text{cutoff frequency } f_C = \frac{1}{2\pi RC} = \frac{1}{2\pi \cdot 10^3 \times 10^{-6}} = \frac{10^3}{2\pi} \text{ Hz}$$

$$\omega_C = 2\pi f_C = 10^3 \text{ rad/s}$$

e) Find the transmission or gain at $\omega/\omega_0 = 0.1$, $\omega/\omega_0 = 1$ and at $\omega/\omega_0 = 10$

$$\textcircled{e} \quad \text{Transmission} = \frac{1}{\sqrt{1+(\frac{\omega}{\omega_0})^2}}$$


$$\frac{\omega}{\omega_0} = 0.1 \Rightarrow T = \frac{1}{\sqrt{1+0.01}} = 0.9901$$

$$\frac{\omega}{\omega_0} = 1 \Rightarrow T = \frac{1}{\sqrt{2}} = 0.707$$


$$\frac{\omega}{\omega_0} = 10 \Rightarrow T = \frac{1}{\sqrt{1+100}} = 0.099$$

f) Plot magnitude response, $|T(j\omega)|$ vs. ω/ω_0 Assume that the capacitor is at a zero state initially


$$VC(t=0) = V(t=0) = 0$$

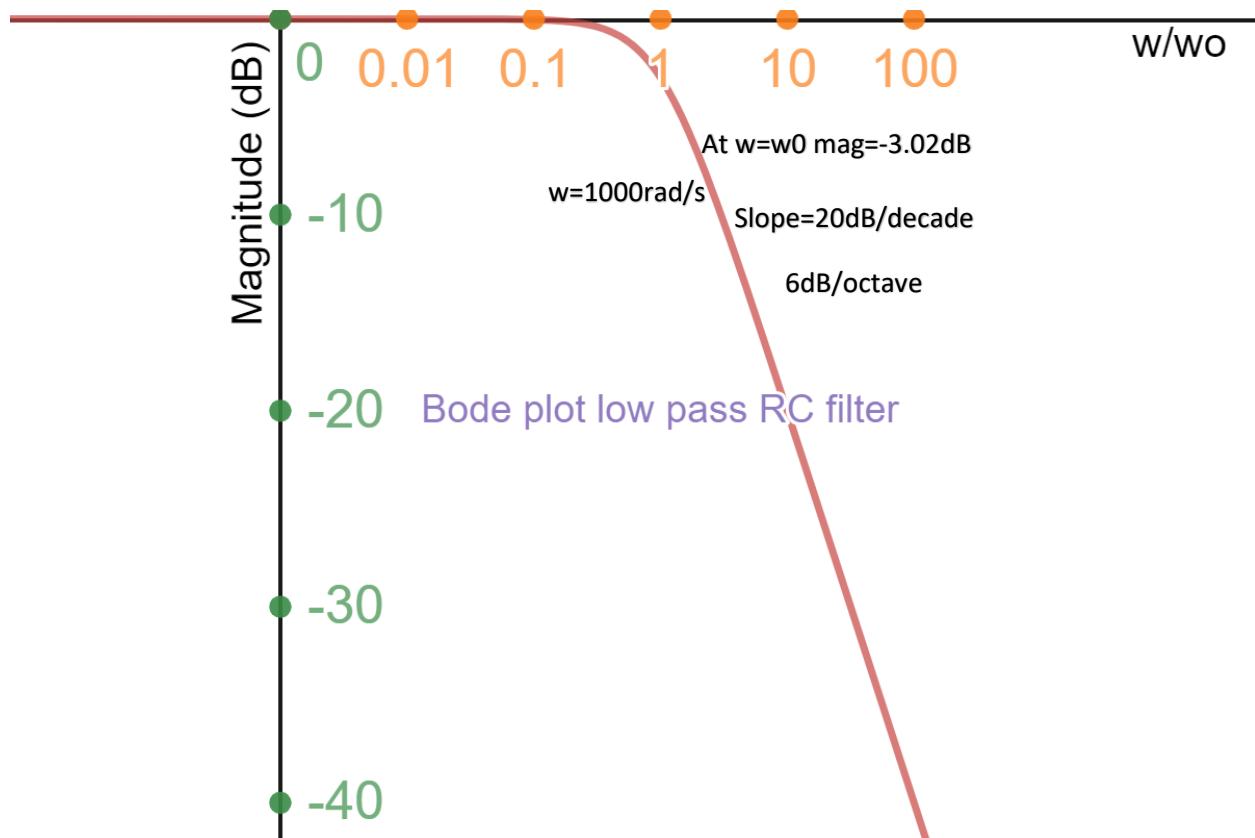

Question 11

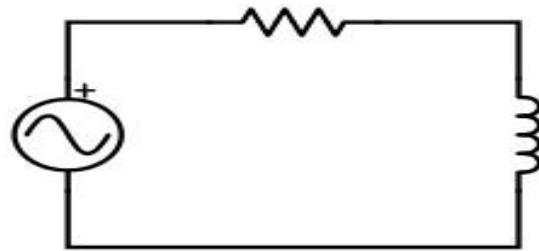

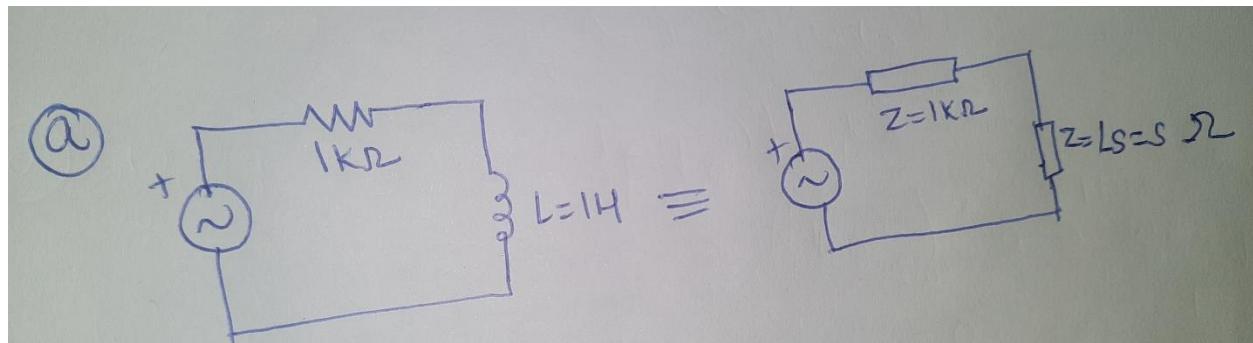a) Draw s-domain transformed circuit for the filter.



b) Find transfer function in s-domain i.e $T(s) = V_o(s)/V_i(s)$.

$$\textcircled{b} \quad T(s) = \frac{V_o}{V_i} = \frac{V_L}{V_L + V_R} = \frac{Z_L}{Z_L + Z_R} = \frac{ls}{R+ls}$$

c) Hence find transfer function for physical frequencies i.e $T(j\omega)$ by $s = j\omega$ and derive expression for magnitude response

$$\textcircled{c} \quad T(j\omega) = \frac{Lj\omega}{R+Lj\omega} \Rightarrow |T(j\omega)| = \frac{|Lj\omega|}{|R+Lj\omega|} = \frac{lw}{\sqrt{R^2+l^2w^2}}$$

d) Also calculate the 3-dB frequency or corner frequency ω_0 for the filter.

(d)

$$|T_{j\omega}| = \frac{|L\omega|}{\sqrt{R^2 + L^2\omega^2}}$$

$$20 \log |T_{j\omega}|_{dB} = -3 dB$$

$$\Rightarrow |T_{j\omega}| = \frac{1}{\sqrt{2}}$$

$$\frac{|L\omega|}{\sqrt{R^2 + L^2\omega^2}} = \frac{1}{\sqrt{2}}$$

$$\Rightarrow 2L^2\omega^2 = R^2 + L^2\omega^2$$

$$\Rightarrow R^2 = L^2\omega^2 \Rightarrow \omega = \sqrt{\left(\frac{R}{L}\right)^2} = \frac{R}{L} = 10^3 \text{ rad s}^{-1}$$

$$\therefore \omega_0 = 10^3 \text{ rad s}^{-1}$$

e) Find the transmission or gain at $\omega/\omega_0 = 0.1$, $\omega/\omega_0 = 1$ and at $\omega/\omega_0 = 10$


$$\textcircled{e} \quad |T(j\omega)| = \frac{|w|}{\sqrt{\omega_0^2 + w^2}} = \frac{1}{\sqrt{(\frac{\omega_0}{\omega})^2 + 1}}$$

$$\text{if } \frac{\omega}{\omega_0} = 0.1 \quad \text{then } |T(j\omega)| = \frac{1}{\sqrt{1+100}} = 0.099$$

$$\text{if } \frac{\omega}{\omega_0} = 1 \quad \text{then } |T(j\omega)| = \frac{1}{\sqrt{2}} = 0.707$$

$$\text{if } \frac{\omega}{\omega_0} = 10 \quad \text{then } |T(j\omega)| = \frac{1}{\sqrt{1+0.01}} = 0.9901$$


f) Plot magnitude response, $|T(j\omega)|$ vs. ω/ω_0

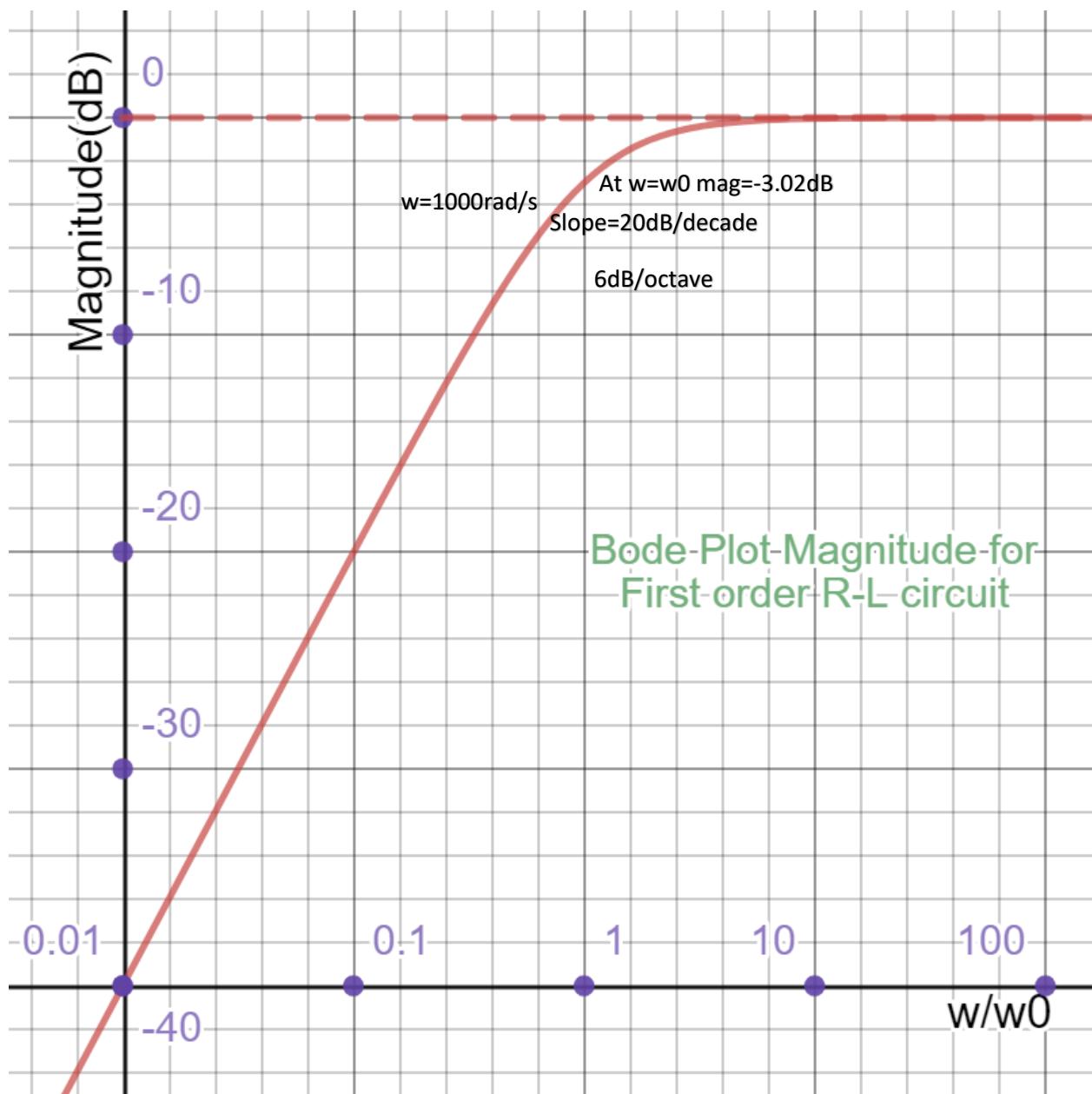

12. For a second-order low pass filter derived by cascading two first order RC low pass filter stage connected through an isolator or buffer stage

with Gain, $A_v = 1$ as shown below. Assume that the capacitor is at a zero state initially i.e. $V_C(t=0) = 0 \text{ V}$.

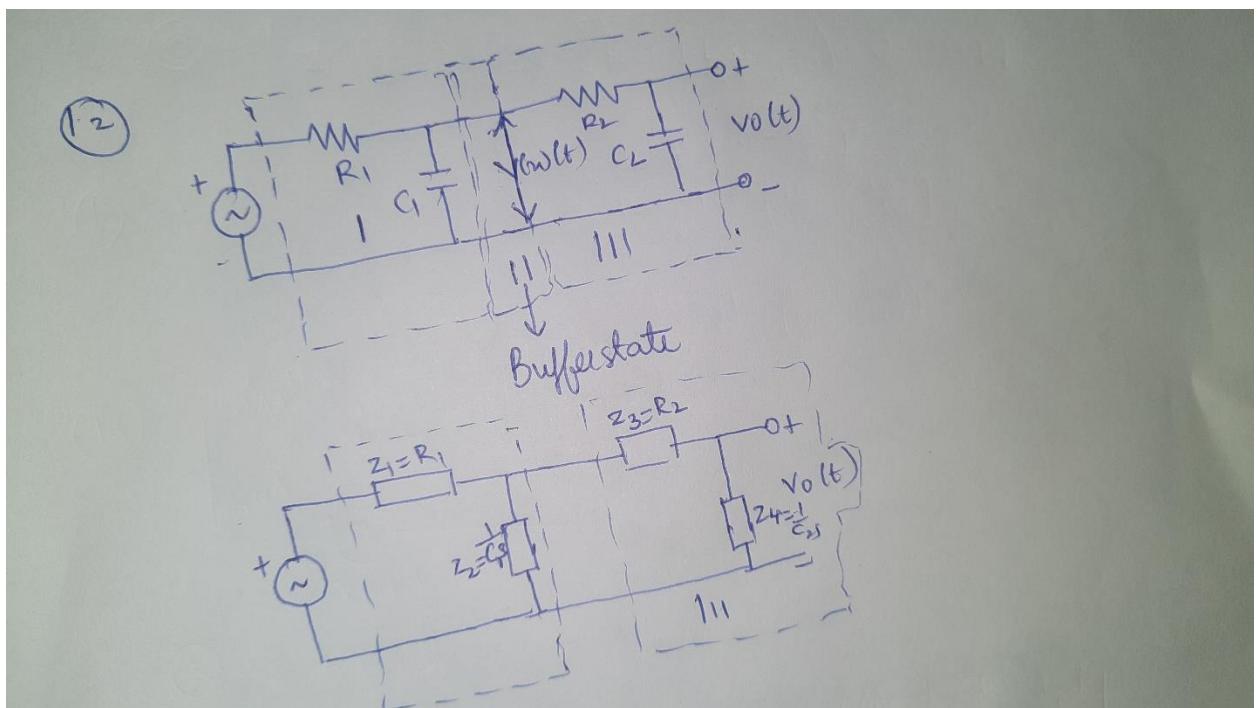(a) Draw s-domain transformed circuit for the filter.



b) Find transfer function in s-domain for Stage (I), Stage (II) and overall transfer function i.e. $T_1(s) = V_x(s)/V_1(s)$, $T_{11}(s) = V_0(s)/V_x(s)$ and $T(s) = V_o(s)/V_i(s)$ respectively

$$\begin{aligned}
 \textcircled{b} \quad v_{(n)}(t) &= \frac{v_i(t) \times Z_{C_1}}{Z_{C_1} + Z_R} \\
 \therefore T_1(s) &= \frac{\frac{1}{C_1 s}}{\frac{1}{R_1} + \frac{1}{C_1 s}} = \frac{1}{R_1 C_1 s + 1} \\
 v_o(t) &= \frac{v_n(t) Z_{C_2}}{Z_{C_2} + Z_{R_2}} \Rightarrow T_2(s) = \frac{1}{R_2 s + 1} \\
 T(s) &= T_{11}(s) \times T_1(s) = \left(\frac{1}{R_1 C_1 s + 1} \right) * \left(\frac{1}{R_2 s + 1} \right)
 \end{aligned}$$

c) Hence find transfer function for physical frequencies i.e $T(j\omega)$ by $s = j\omega$ and derive expression for magnitude response, $|T(j\omega)|$

$$\begin{aligned}
 \textcircled{c} \quad T(j\omega) &= \frac{1}{R_1 C_1 j\omega + 1} * \frac{1}{R_2 C_2 j\omega} \\
 |T(j\omega)| &= \frac{1}{\sqrt{1 + R_1^2 C_1^2 \omega^2}} \times \frac{1}{\sqrt{1 + R_2^2 C_2^2 \omega^2}}
 \end{aligned}$$

d) Also calculate the corner frequency, ω_0 for the filter

$$\textcircled{a} \quad |T(j\omega)| = \frac{1}{\sqrt{1+10^{-6}\omega^2} \sqrt{1+10^{-6}\omega^2}} = \frac{1}{1+10^{-6}\omega^2}$$

ω_0 is the frequency for which $|T(j\omega)| \text{dB} = -6 \text{ dB}$

$$\Rightarrow 20 \log(|T(j\omega)|) = -6.02$$

$$\Rightarrow \log|T(j\omega)| = -0.301$$

$$\Rightarrow |T(j\omega)| = \frac{1}{2}$$

$$\Rightarrow 1+10^{-6}\omega^2 = 2 \Rightarrow \omega = 10^3 \text{ rad s}^{-1}$$

$$\therefore \text{corner frequency } (\omega_0) = 10^3 \text{ rad s}^{-1}$$

e) Find the transmission or gain at $\omega/\omega_0 = 0.1$, $\omega/\omega_0 = 1$ and at $\omega/\omega_0 = 10$


$$\textcircled{e} \quad \frac{\omega}{\omega_0} = 0.1 \Rightarrow |T(j\omega)| = \frac{1}{\left(\sqrt{1+\frac{\omega^2}{\omega_0^2}}\right)^2} = \frac{1}{1+\frac{\omega^2}{\omega_0^2}} = \frac{1}{1+0.01} = 0.99$$

$$\frac{\omega}{\omega_0} = 1 \Rightarrow |T(j\omega)| = \frac{1}{1+1} = 0.5$$

$$\frac{\omega}{\omega_0} = 10 \Rightarrow |T(j\omega)| = \frac{1}{1+100} = 0.0099$$


f) Plot magnitude response, $|T(j\omega)|$ vs. ω/ω_0 . Assume that the capacitor is at a zero state initially i.e. $V_{C1}(t=0) = V_{C2}(t=0) = 0$

V , also $R_1 = R_2$, $C_1 = C_2$

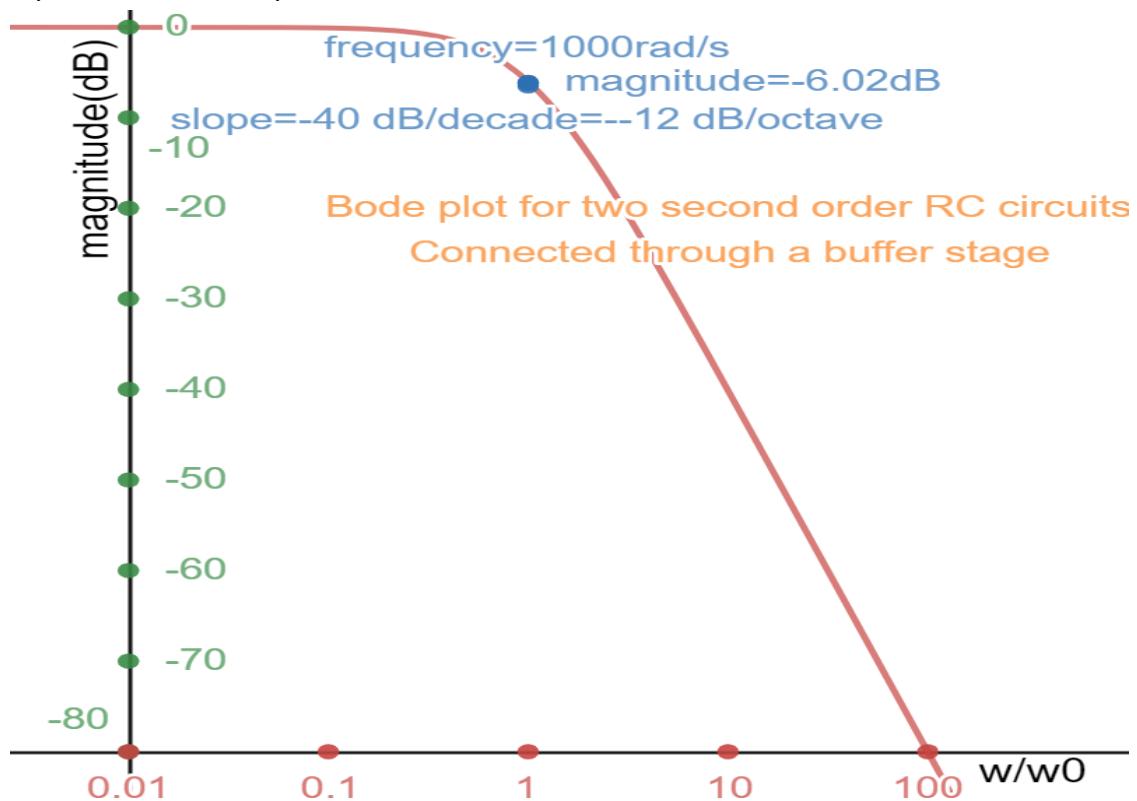

Question 13

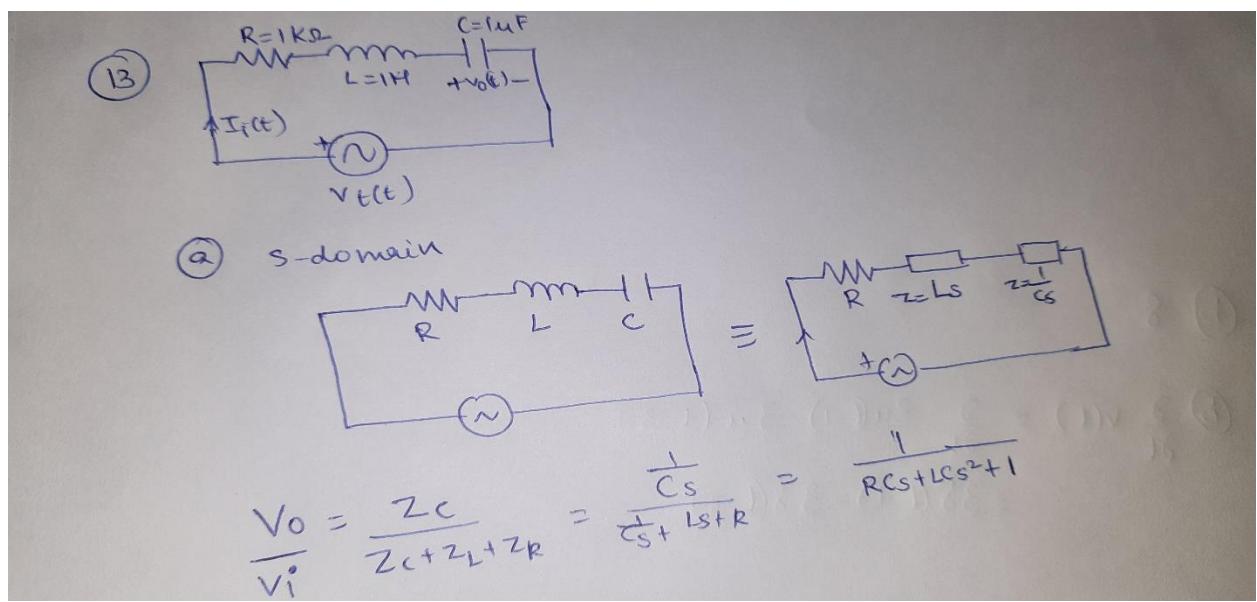a) Draw s-domain transformed circuit for the resonator



b) Find impedance offered by the circuit in s-domain i.e.

$$Z(s) = V_1(s) / I_1(s)$$

(b) $Z_s = Z_R + Z_L + Z_C$

$$= R + Ls + \frac{1}{Cs}$$

c) Hence find impedance for physical frequencies i.e $Z(j\omega)$ by considering $s = j\omega$ and derive expression for magnitude response, $|Z(j\omega)|$

(c) $|Z(j\omega)| = |R + L\omega j + \frac{1}{Cj\omega}|$

$$= \sqrt{|R + L\omega j - \frac{1}{C\omega} j|^2}$$

$$= \sqrt{R^2 + \left(L\omega - \frac{1}{C\omega}\right)^2}$$

(d) Determine the resonant frequency, ω_0 where the circuit offers purely resistive impedance


(d) ω_0 is such that $|Z(j\omega)| = R$

$$\Rightarrow R = \sqrt{R^2 + \left(L\omega - \frac{1}{C\omega}\right)^2} \Rightarrow L\omega - \frac{1}{C\omega} = 0 \Rightarrow \omega_0 = \frac{1}{\sqrt{LC}}$$


$$= \frac{1}{\sqrt{10^{-6}}} = 10^3 \text{ rad/s}$$

(e) Plot $|Z(j\omega)|$ and $|Y(j\omega)| = 1/Z(j\omega)$ versus normalised frequency, ω/ω_0 . Assume that the inductor and capacitor are at zero state initially i.e. $I_L(t=0) = 0 A$ and $V_C(t=0) = 0$

$$\begin{aligned}
 \textcircled{e} \quad |Z(j\omega)| &= \sqrt{R^2 + \left(L\omega - \frac{1}{C\omega}\right)^2} \\
 &= \sqrt{10^6 + \left(\omega - \frac{10^6}{\omega}\right)^2} \\
 &= 10^3 \sqrt{1 + \left(\frac{\omega}{10^3} - \frac{10^3}{\omega}\right)^2} \\
 &= 10^3 \sqrt{1 + \left(\frac{\omega}{\omega_0} - \frac{\omega_0}{\omega}\right)^2}
 \end{aligned}$$

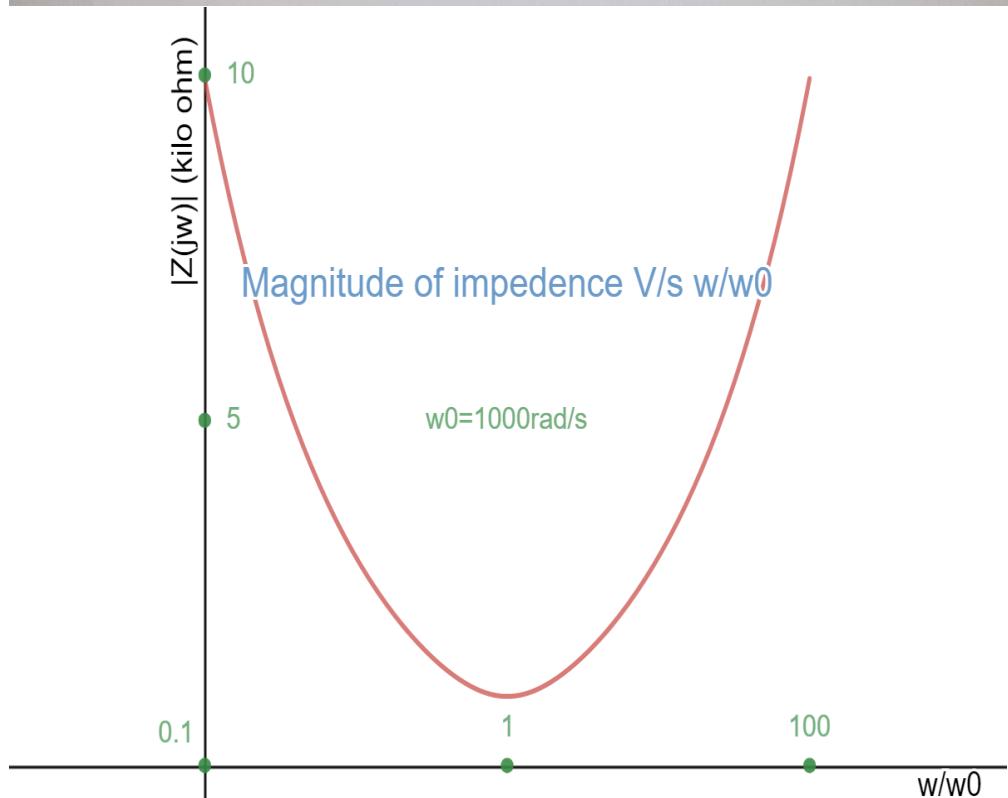

Plot of Impedance versus w/w_0

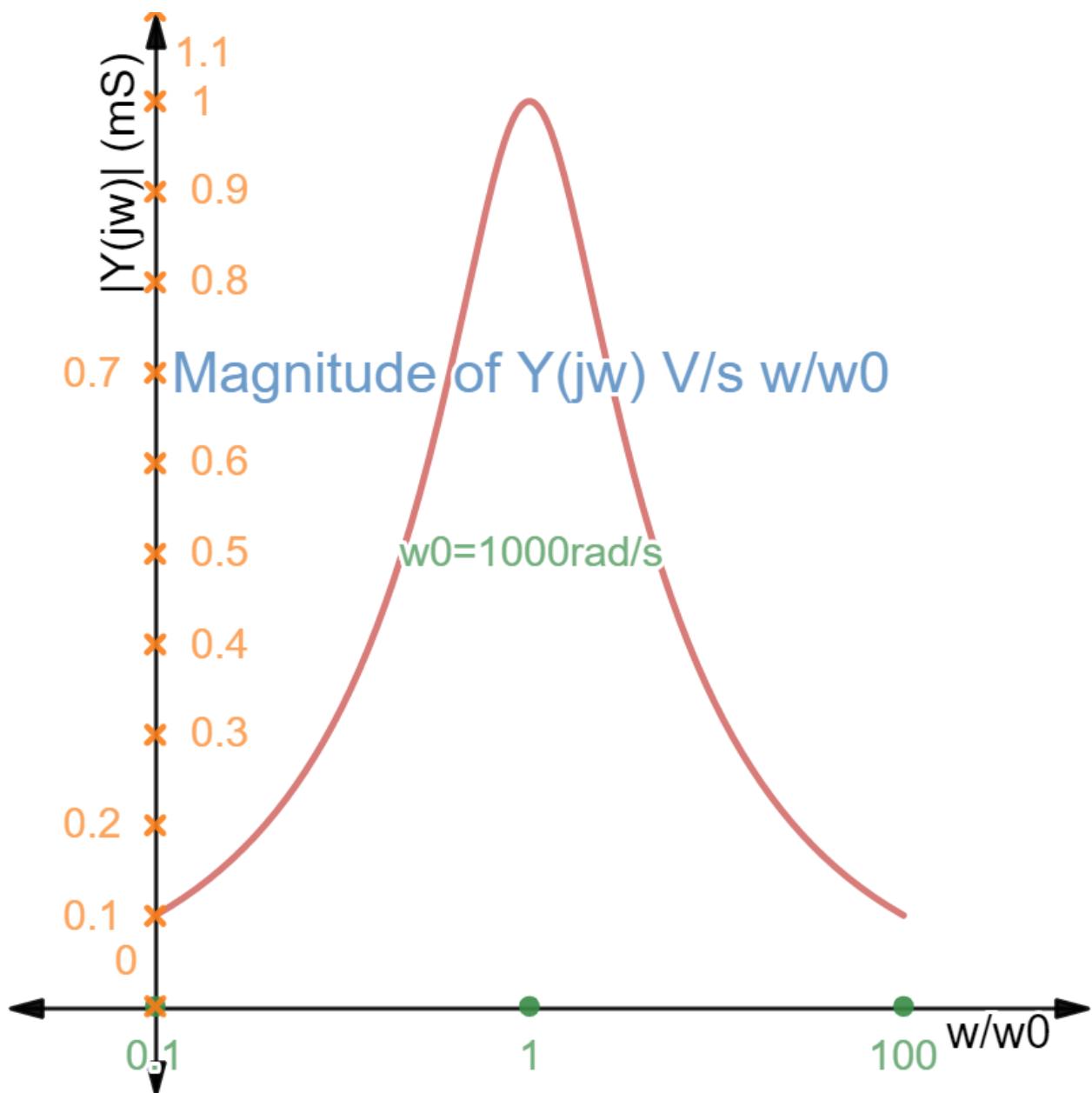

Plot of Admitance versus w/w_0

Thank you!!